
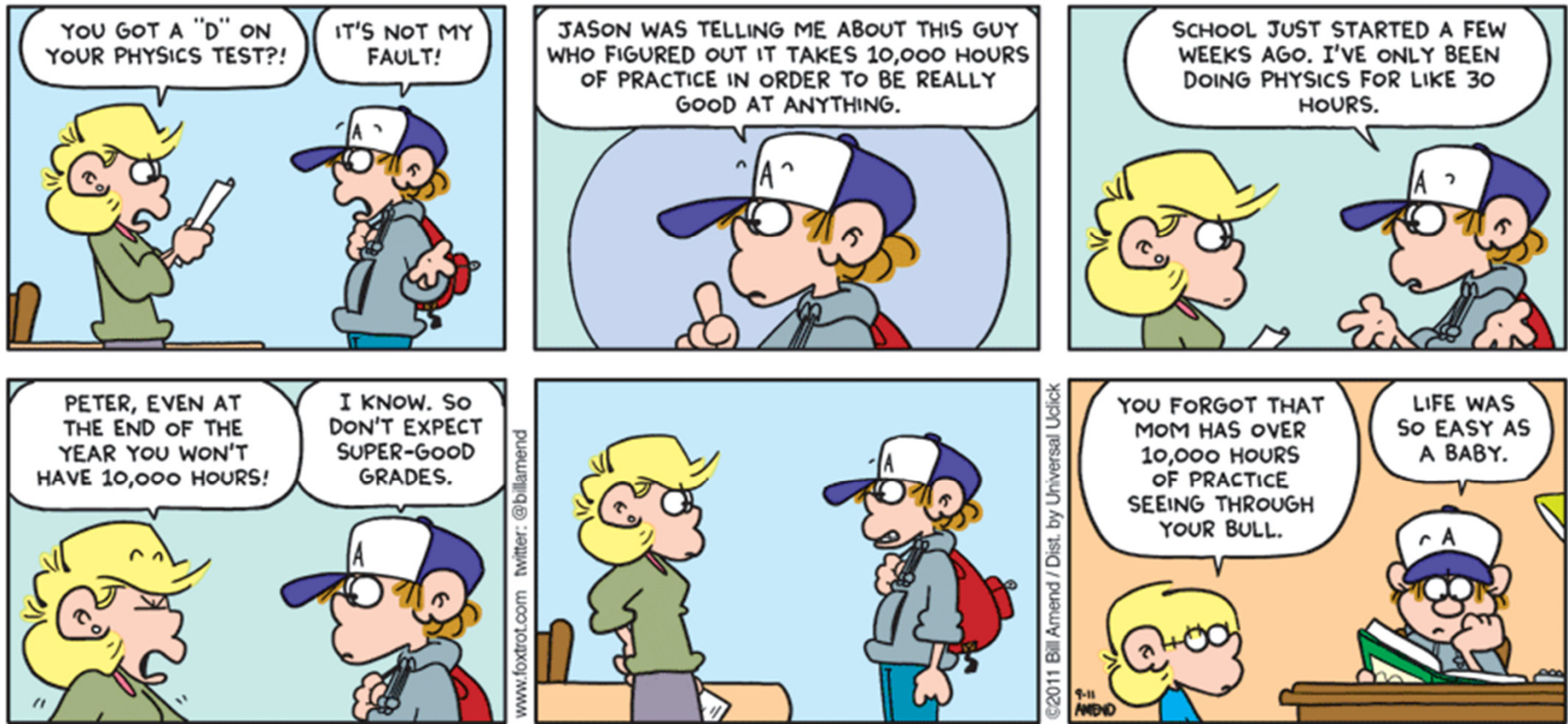


From the "Foxtrot" comic:

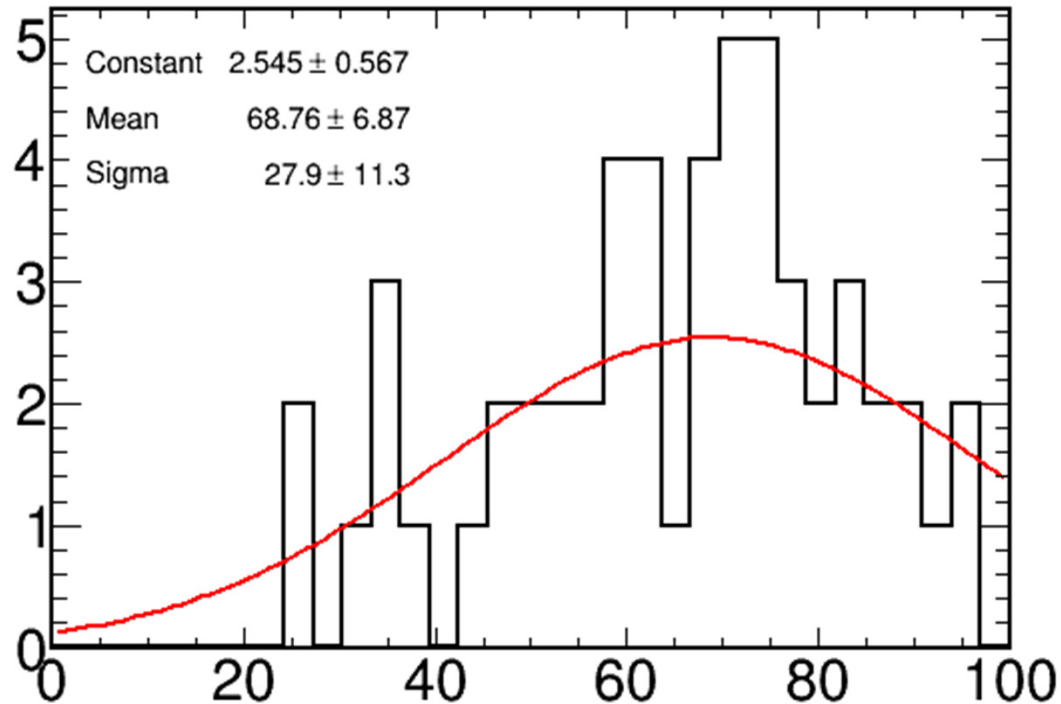

Fun fact: cartoonist Bill Amend took the unusual career path of turning a physics major into a cartooning career


Scores on Test



- 70+: Doing fine!
 - 60's: doing ok, some things you need to figure out
 - 50's: meh
 - Lower: time to worry
- (the red line and fit parameters show a Gaussian fit failing miserably)*

Best guess at a “curve” (*ie*, turning percents into letter grades) is online, and uses your total score (see next slide)

Total Scores

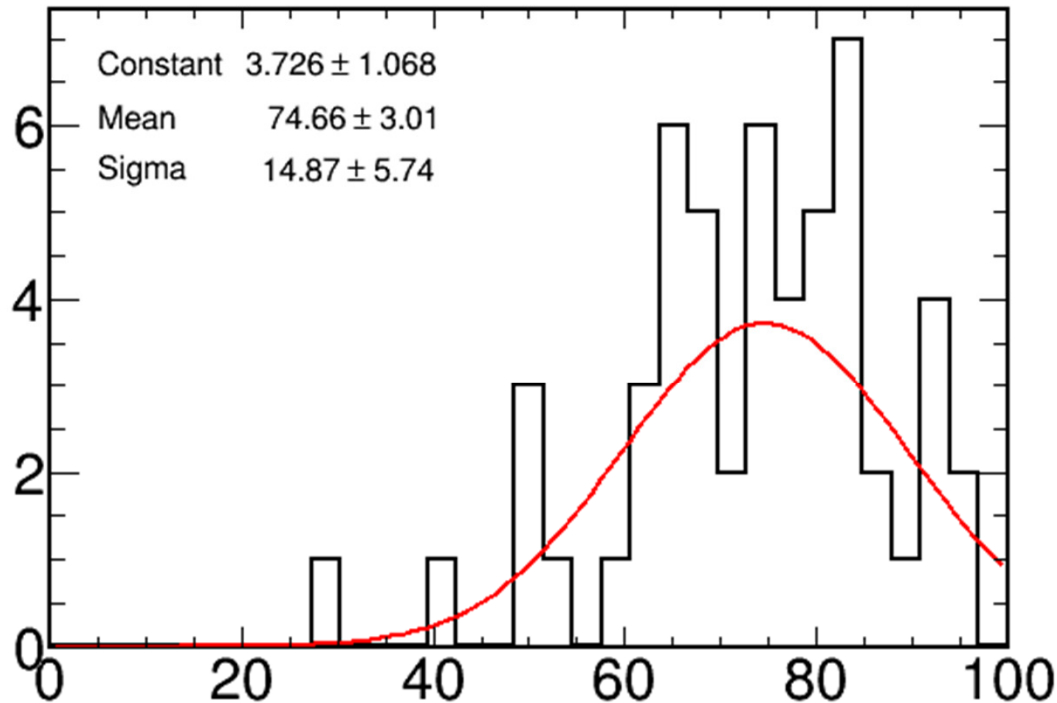

eGradebook total calculation done with:


- Dropping lowest thing in each of: HW, In class thing, clicker, online HW, online RQ


Following the recipe on the “grades” link, a letter grade is posted.

If the semester was done today, that’s what you’d get.

Someone will now ask: “Was this curved?”.

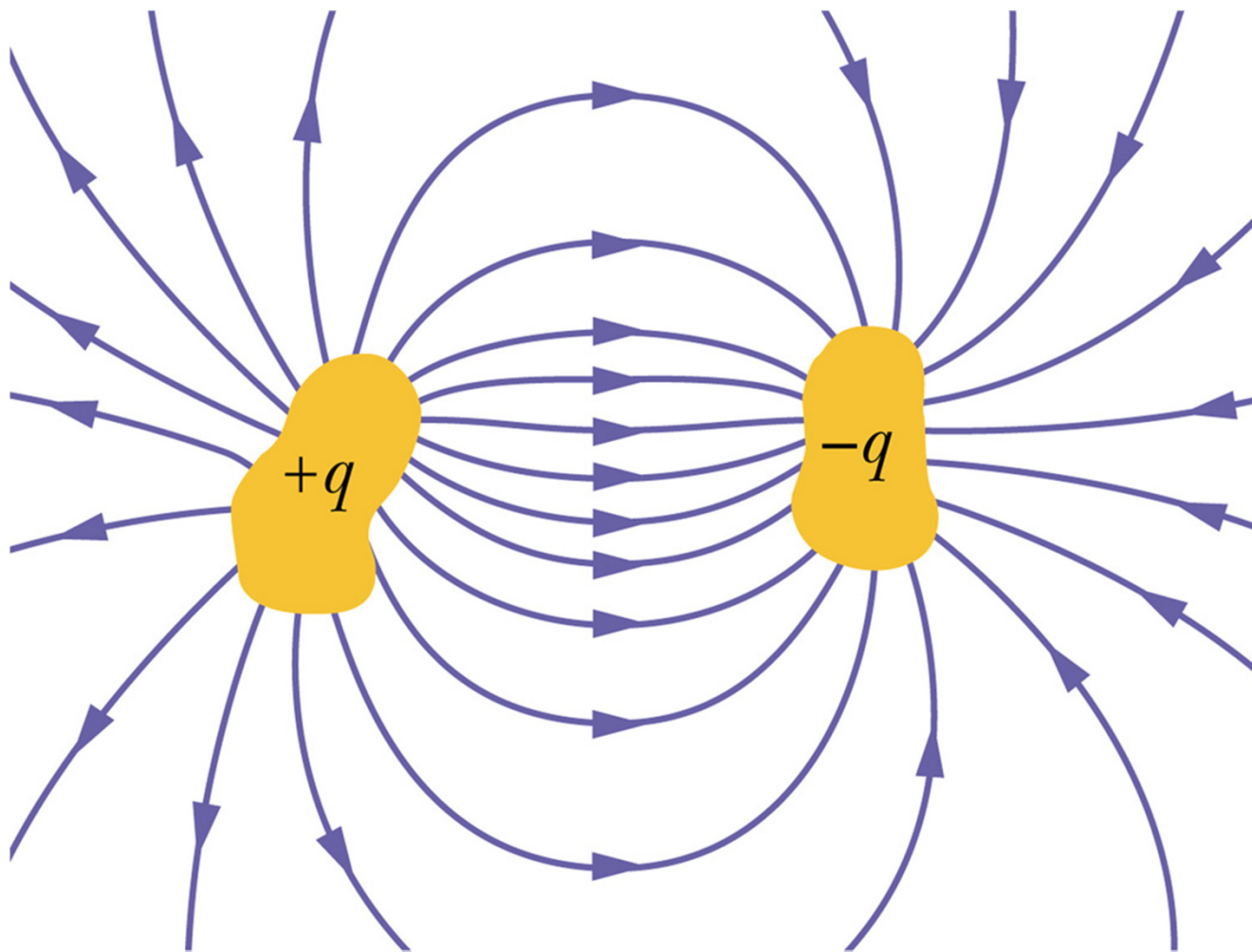Answer: the very act of turning some percent grade into some letter grade is exactly what “curving” does. So, yes.



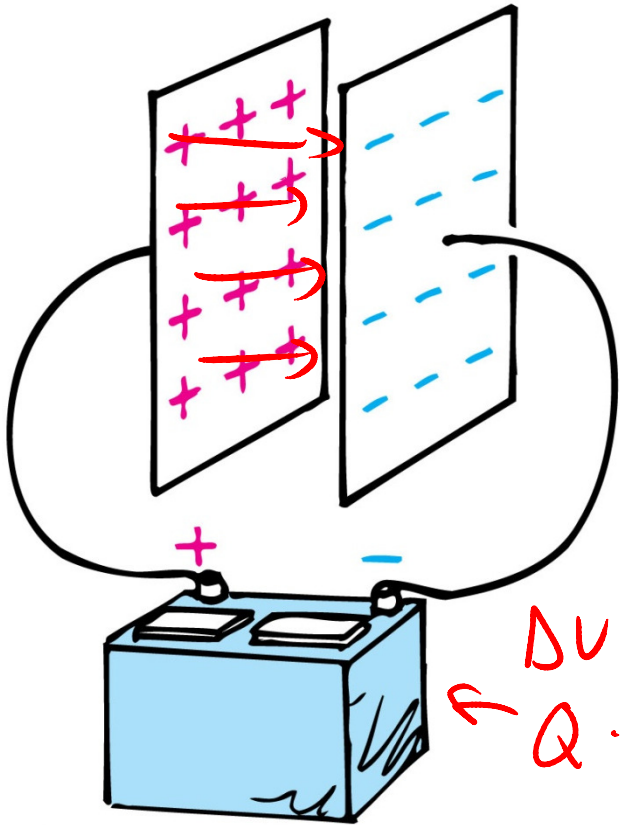


"Capacitance"

$$q = CV$$


$$1 \text{ Farad} = F = \frac{C}{V}$$

ΔV - holding
 Q - producing
 machine


© 2009 Pearson Education, Inc.


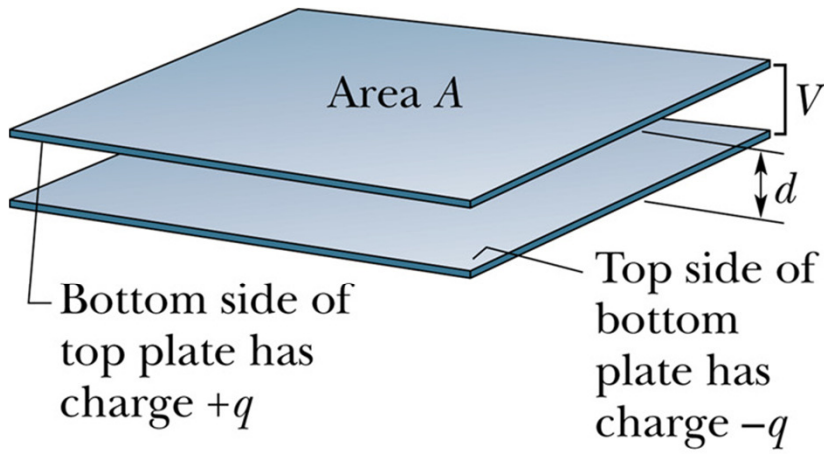


(a)


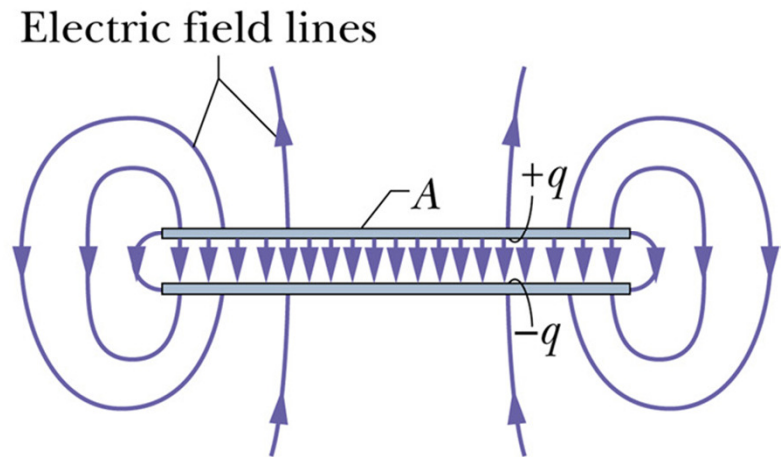


(b)


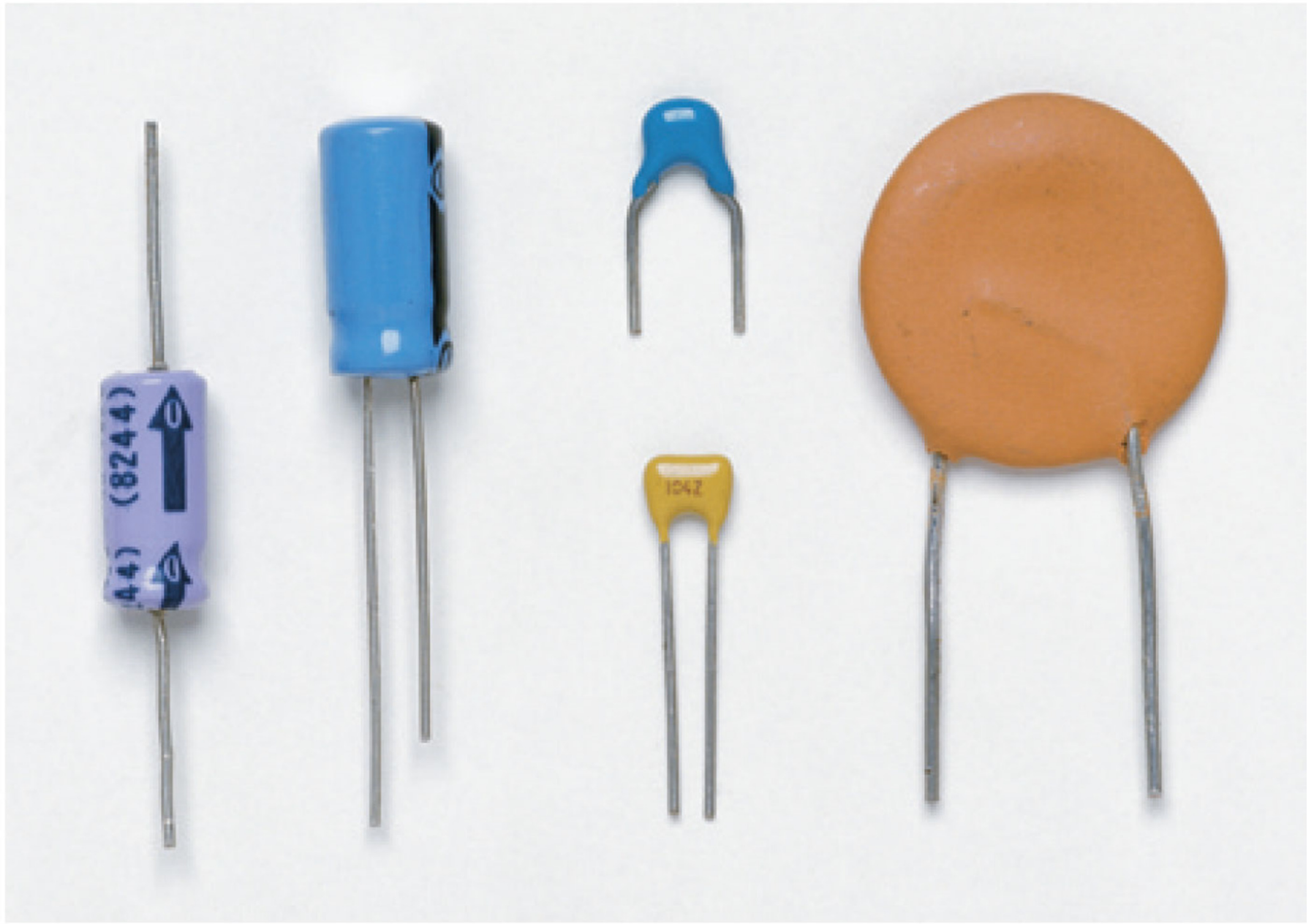


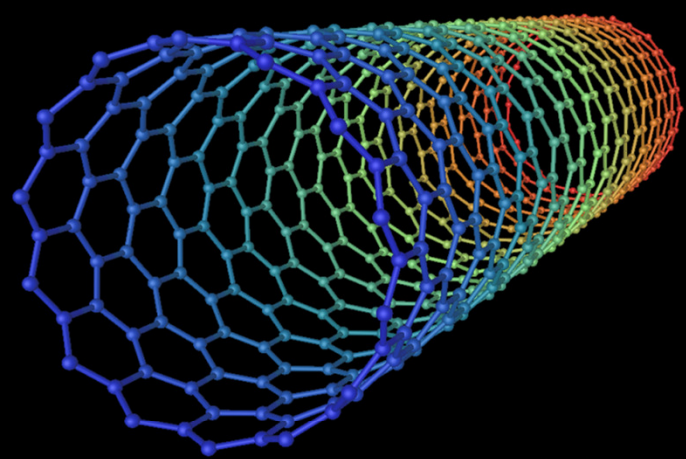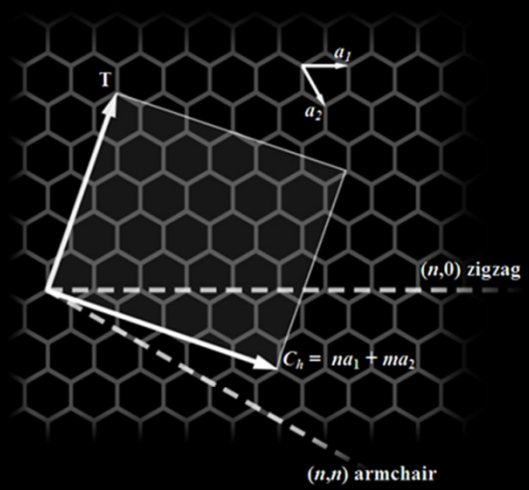


(0,10) nanotube
(zig-zag)

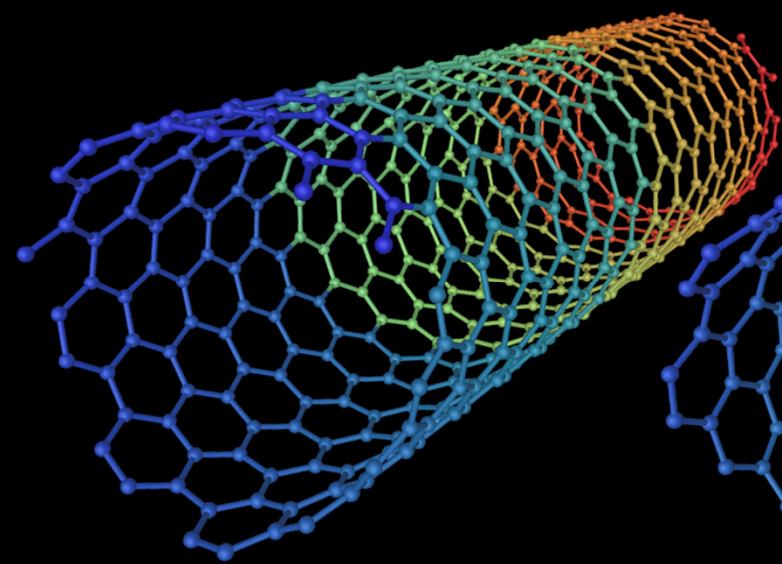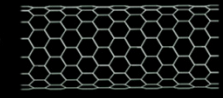


(7,10) nanotube
(chiral)

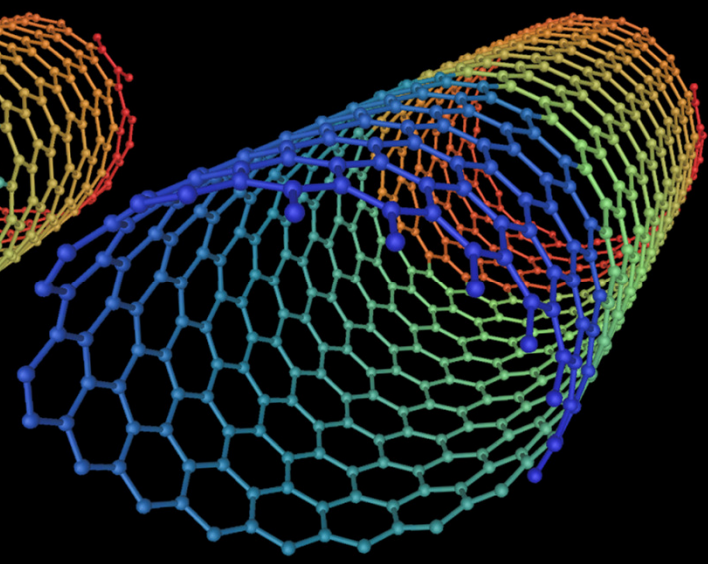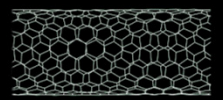

(10,10) nanotube
(armchair)

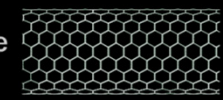

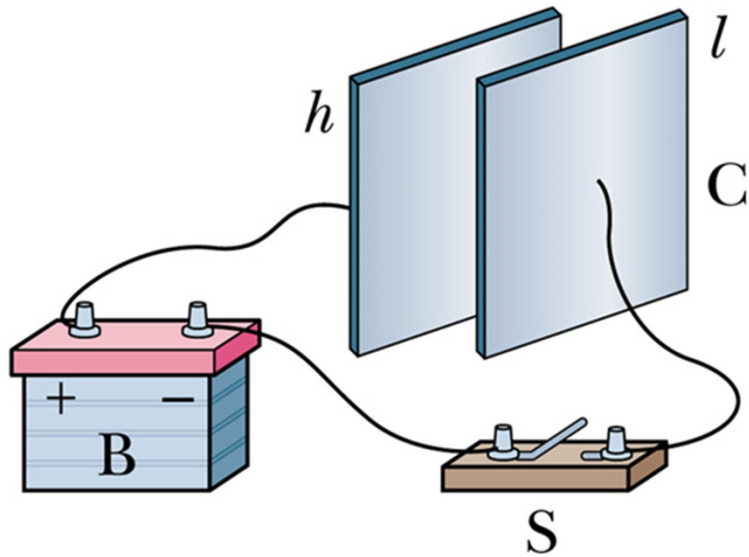


(a)


$$Q = CV$$

$C = \text{Capacitance}$

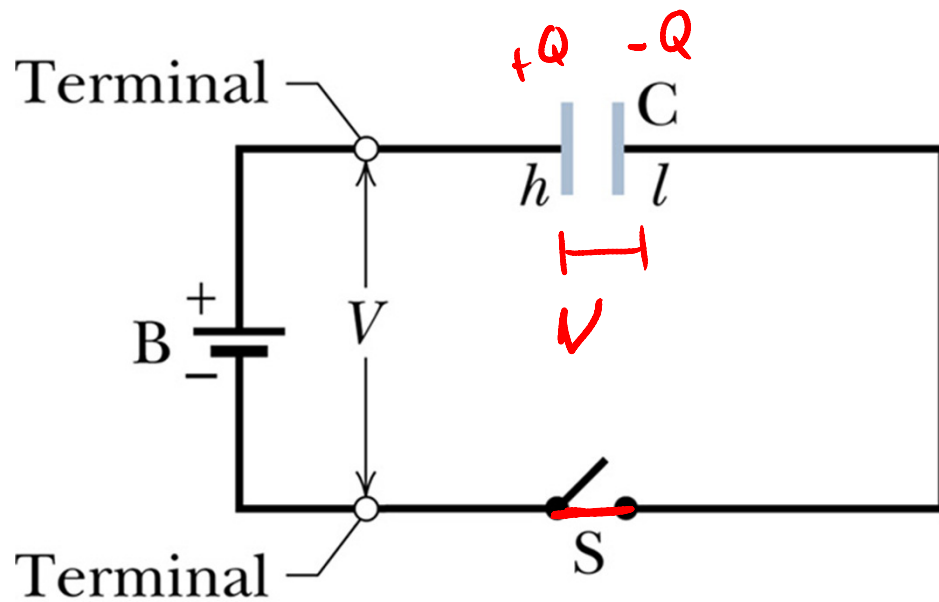
$$\text{Farad} = \frac{\text{Coulombs}}{\text{Volt}}$$



(b)

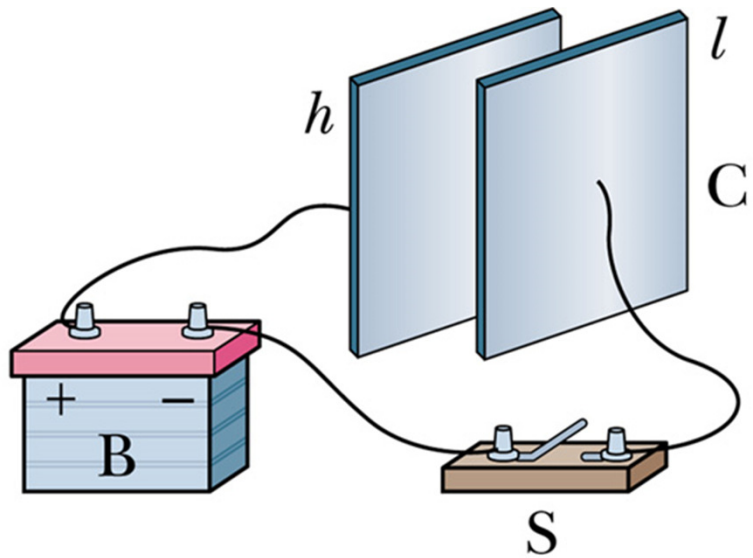




(a)

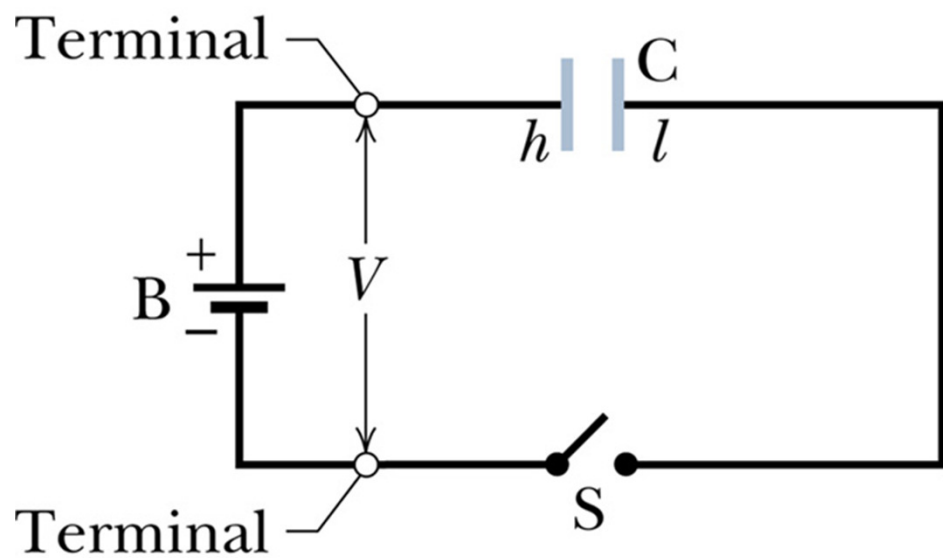

(b)

$$C = \frac{q}{V}$$

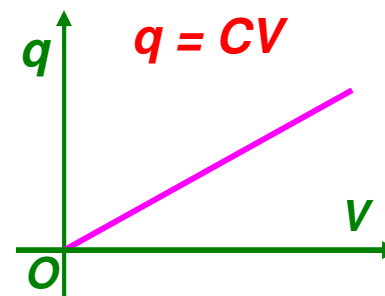

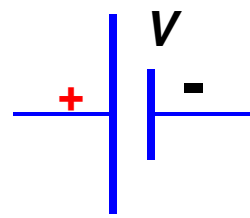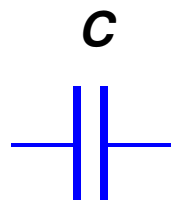

So, what is this proportionality constant C for this set of parallel plates?
 Let's work it out using Gauss' Law $C = Q/V$


$$\int \vec{E} \cdot d\vec{A} = q_{enc} / \epsilon_0$$

$$\int E |dA| \cos \theta = q_{enc} / \epsilon_0$$

$$E \int dA = EA = q_{enc} / \epsilon_0$$

$$0 + 0 + 0 + 0 + GA = q_{enc} / \epsilon_0$$

$$E = \frac{q}{\epsilon_0 A}$$

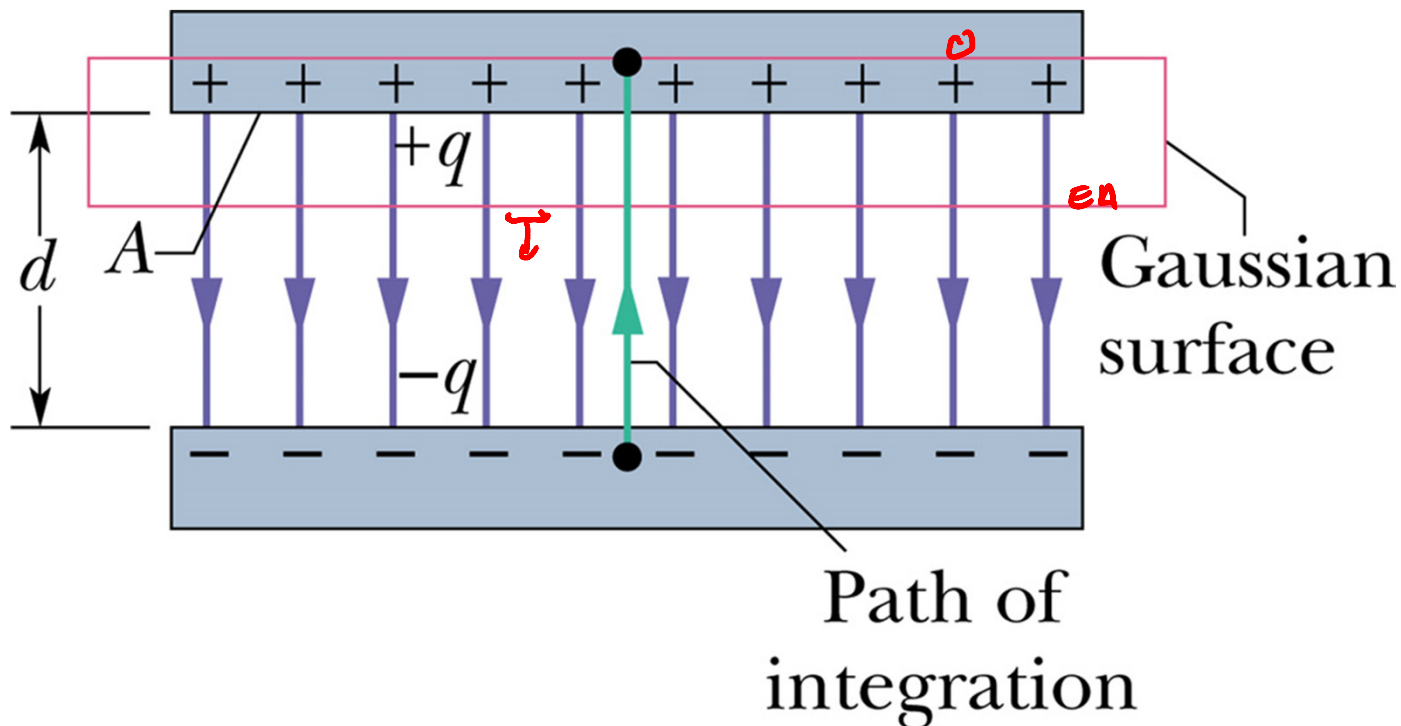

$$E = \frac{Q}{\epsilon_0 A}$$


$$\Delta V = - \int_c^f \vec{E} \cdot d\vec{s}$$
$$= - \int_c^f |E| ds \cos 0^\circ$$

$$\Delta V = E \int_c^f ds = E d$$

$$V = E \cdot d = \frac{Q d}{\epsilon_0 A}$$


$$C = \frac{Q}{V}$$

$$C = \frac{\epsilon_0 A}{d}$$

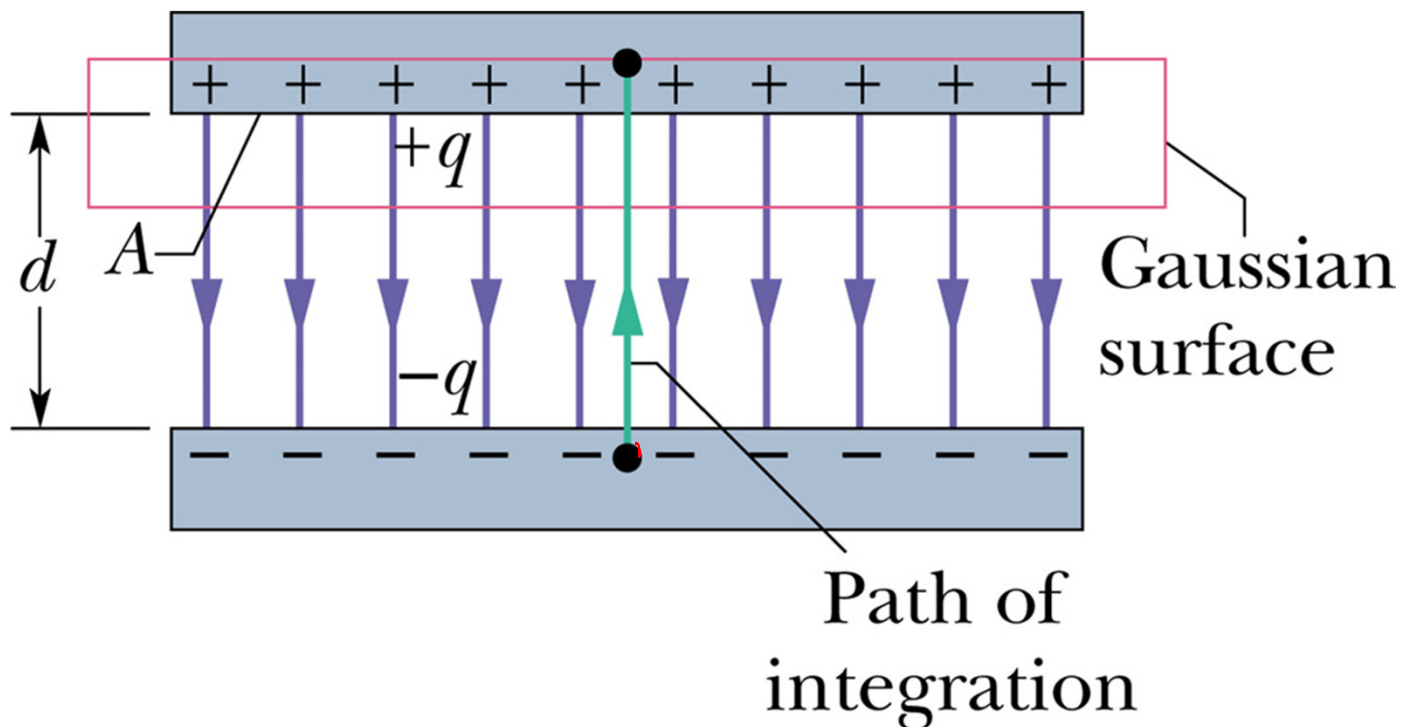

The plates of an isolated parallel plate capacitor with a capacitance C carry a charge Q . What is the capacitance of the capacitor if the charge is increased to $4Q$?

1. $C/2$
2. $C/4$
3. $4C$
4. $2C$
5. C

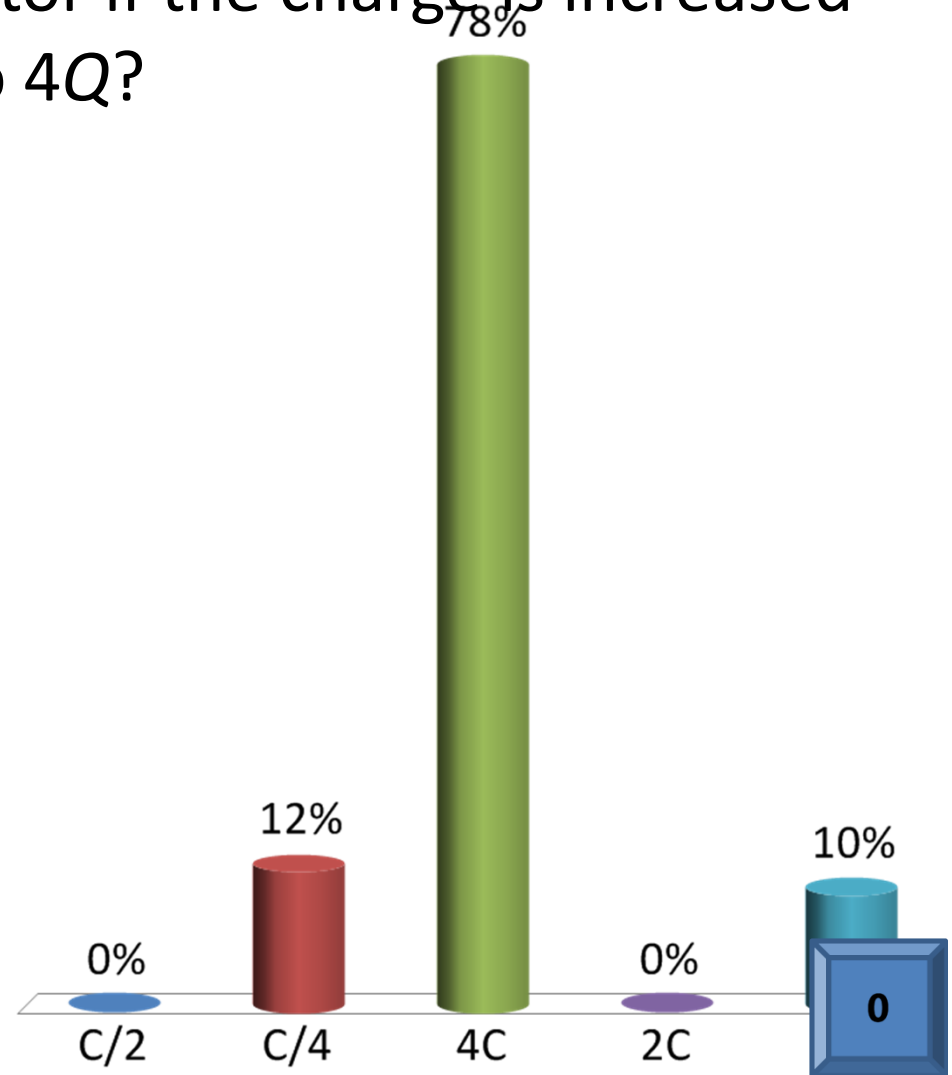

51 of 54


A parallel plate capacitor with plates of area A and plate separation d is charged so that the potential difference between its plates is V . If the capacitor is then isolated and its plate separation is increased to $2d$, what is the potential difference between the plates?

1. 4V
- ✓ 2. 2V
3. V
4. 0.5V
5. 0.25V

$$C = \frac{Q}{V}$$

$$C = \frac{\epsilon_0 A}{d}$$



$$\frac{\epsilon_0 A}{d} = \frac{Q}{V}$$

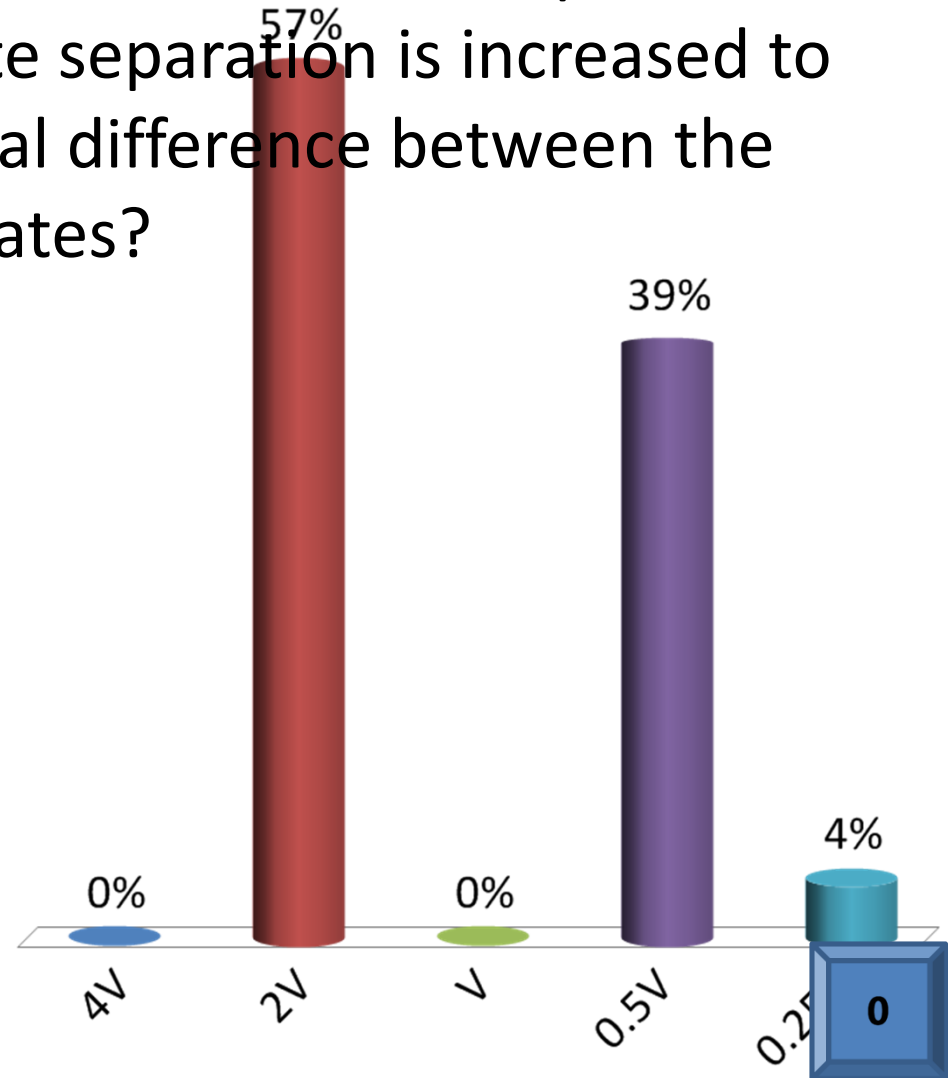


Energy stored in a Capacitor

... and thus, Energy of an electric field
itself.

Fig. 27.6

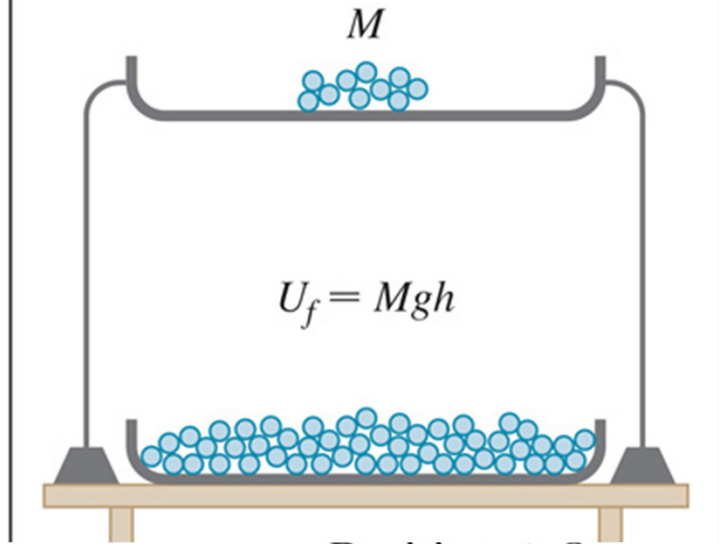
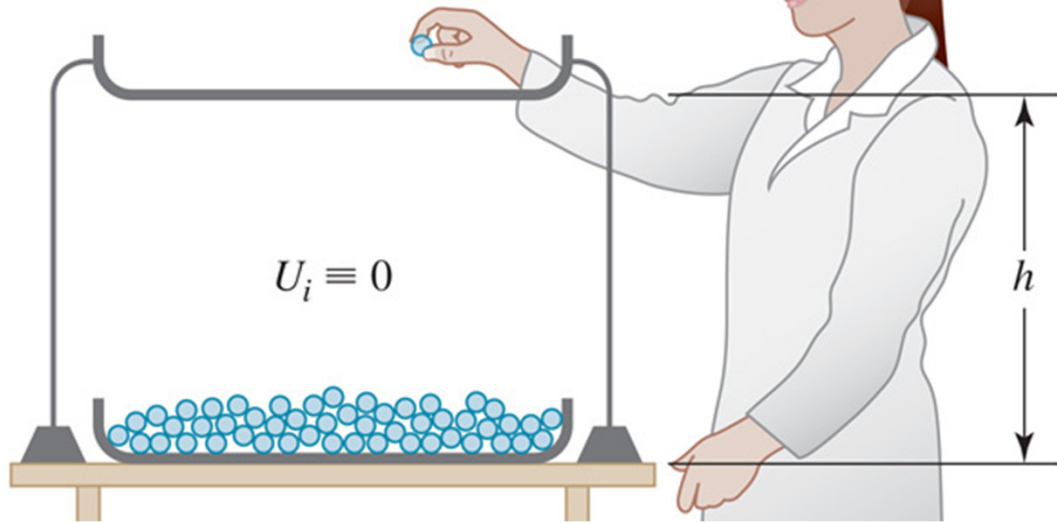


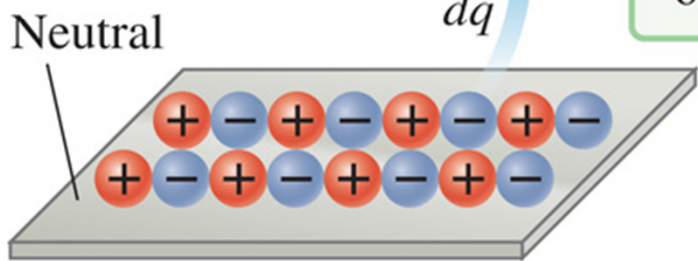Positively charged particles moved one at a time





A. Before

Fig. 27.7

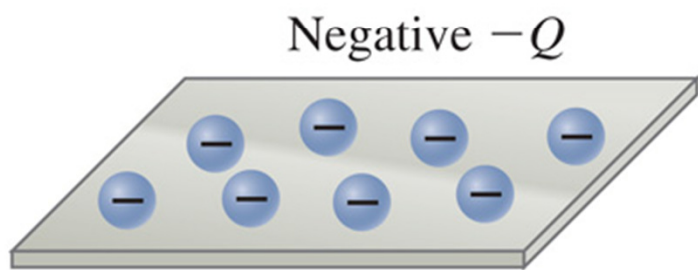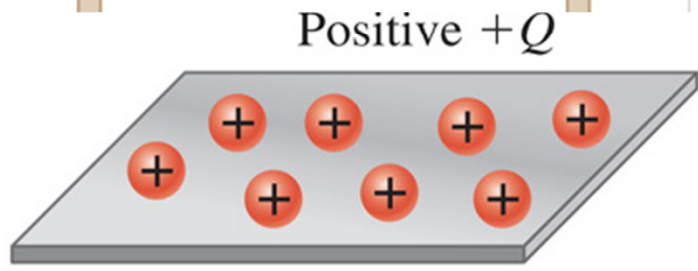

B. After

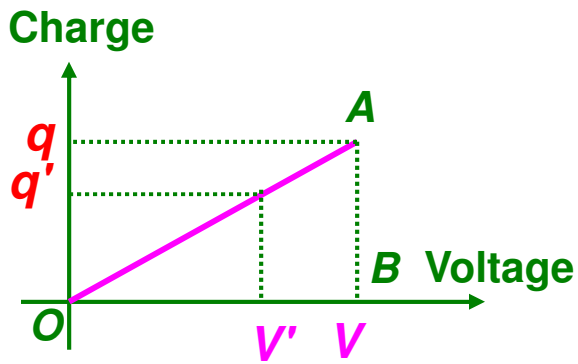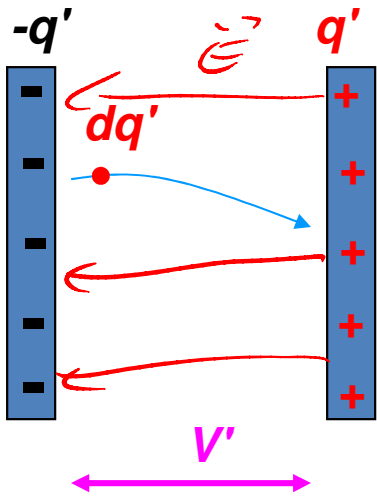

$$dW = V' da' \quad V' = \frac{q'}{C}$$

$$dW = \frac{q' da'}{C}$$

$$\int dW = \int \frac{q' da'}{C} = \frac{1}{C} \int_0^q q' da'$$


$$W = \frac{1}{C} \Big|_0^q \frac{1}{2} q'^2$$

$$U_{cap} = \frac{q^2}{2C}$$

$$q = CV$$

$$U_{cap} = \frac{1}{2} CV^2$$

energy
in
Cap.

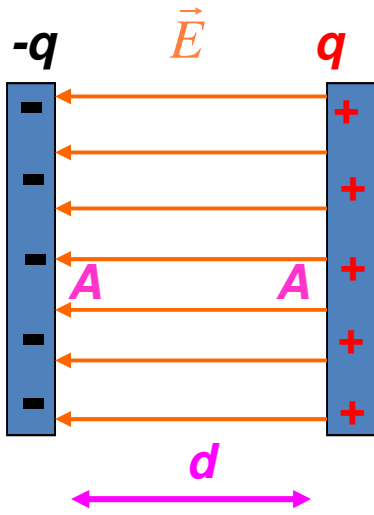

\vec{E} is Uniform

$U / \text{Volume?}$ $\frac{J}{m^3}$

$u = \text{energy density} = \frac{U}{\text{Volume}}$

$$u = \frac{U}{A \cdot d} = \frac{C V^2}{2 A d}$$

$$C = \frac{\epsilon_0 A}{d} \quad (\text{for a 11-plate cap})$$

$$\text{get } u = \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2$$

$$\frac{V}{d} = E \text{ if } E \text{ was constant}$$


$$u = \frac{1}{2} \epsilon_0 E^2$$

The plates of parallel plate capacitor are separated by a distance d and carry a charge of q . The distance between the plates is reduced to $d/2$. How is the energy in the capacitor affected by this change?

- ✓ 1. Energy increases by twice IF CONSTANT V
- 2. Energy increases by four times
- 3. The energy does not change
- 4. Energy decreases to a fourth
- 5. Energy decreases to a half

$$U = \frac{1}{2} C V^2$$
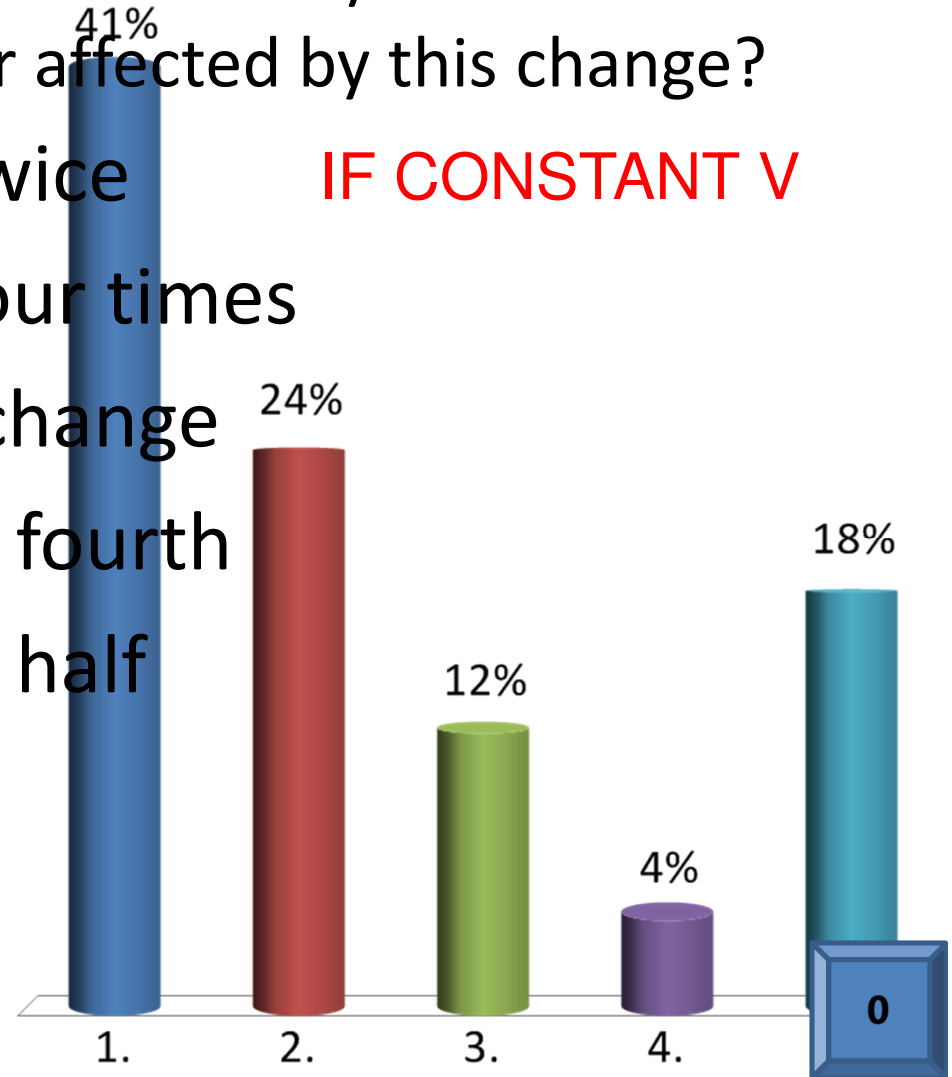
$$C = \frac{\epsilon_0 A}{d} \quad C \rightarrow 2C$$



The plates of parallel plate capacitor are separated by a distance d and carry a charge of q . The distance between the plates is reduced to $d/2$. How is the energy in the capacitor affected by this change?

1. Energy increases by twice
2. Energy increases by four times
3. The energy does not change
4. Energy decreases to a fourth
- ✓ 5. Energy decreases to a half

IF CONSTANT Q

$$U = \frac{Q^2}{2C}$$
$$C \Rightarrow 2x$$



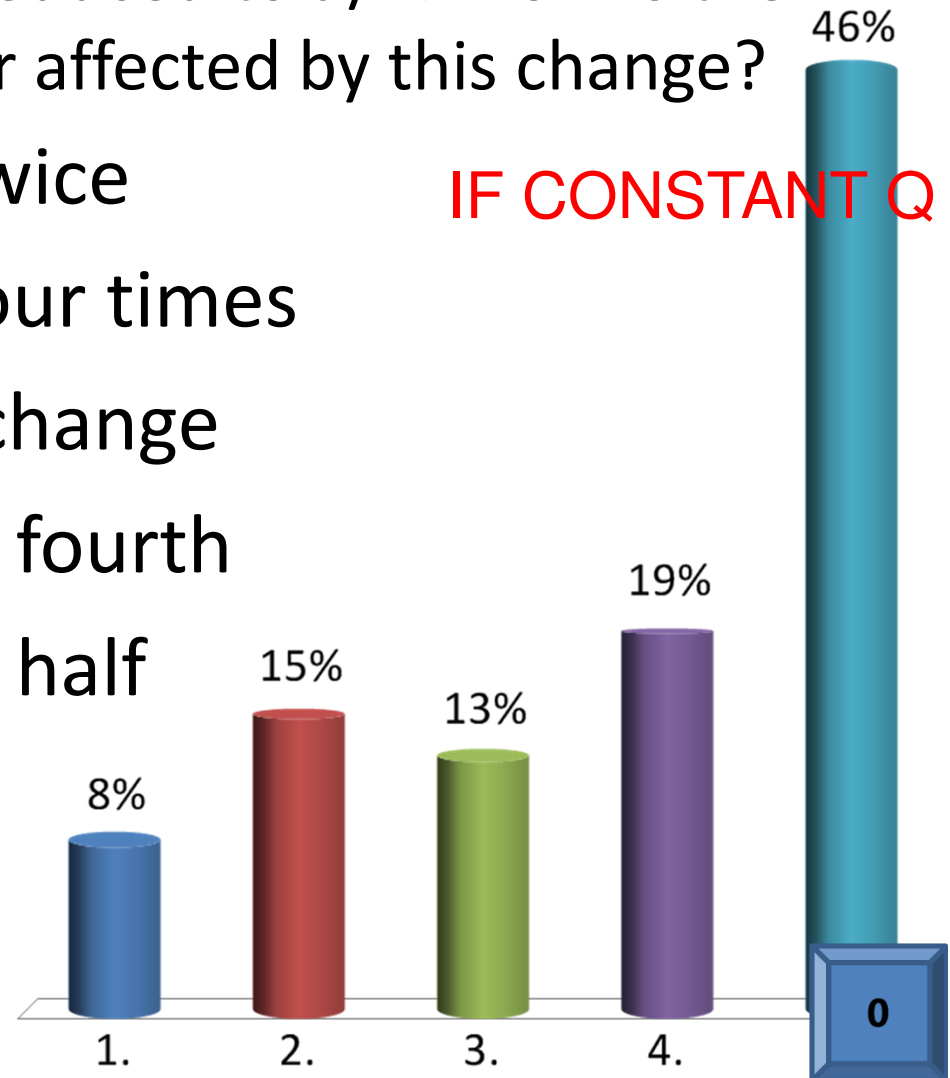


Fig. 27.14

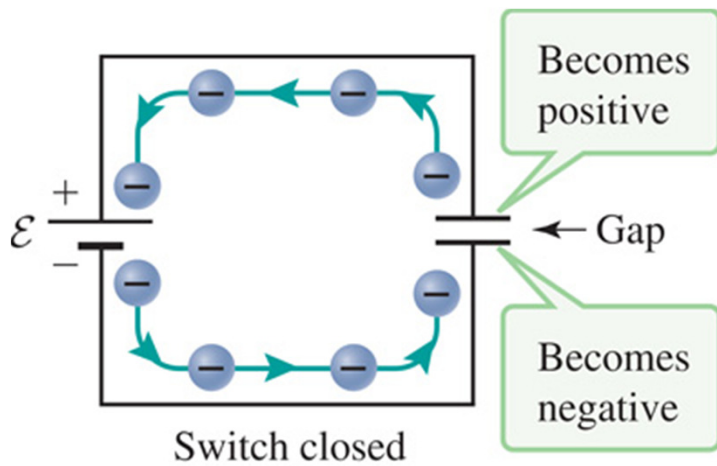

A.

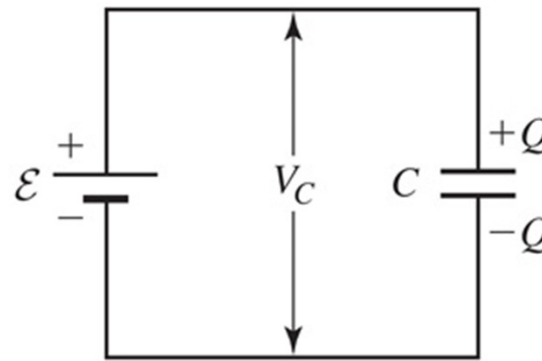

B.

Charged particles continue to build up on plates of capacitor until potential difference between plates of capacitor equals terminal potential:
 $\mathcal{E} = V_C = Q/C.$

Fig. 27.20

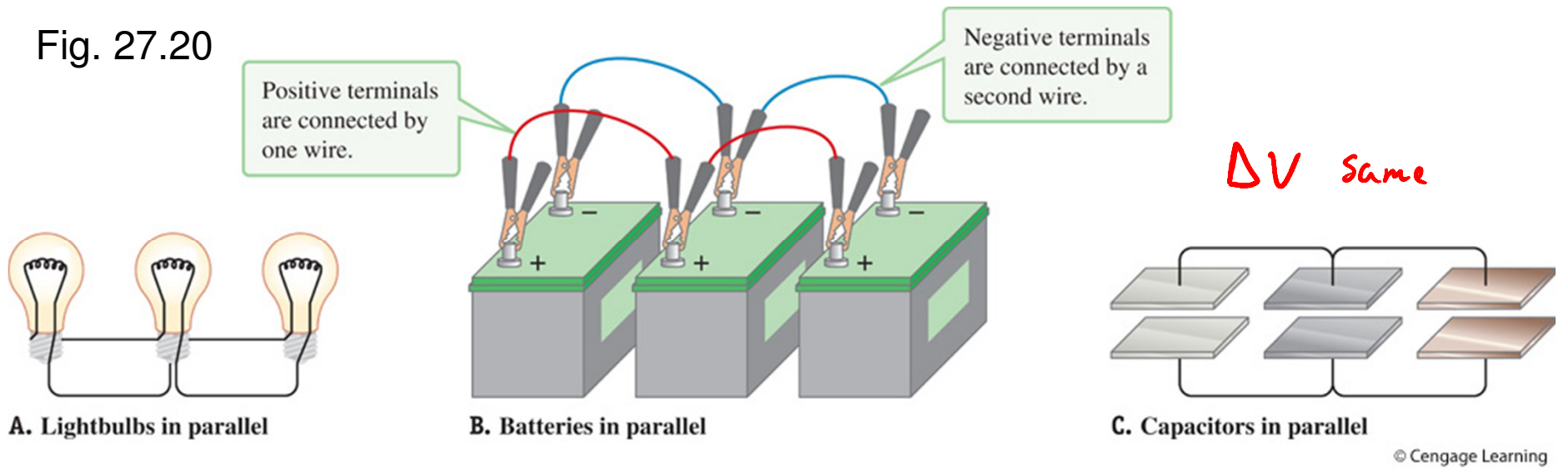


Fig. 27.16



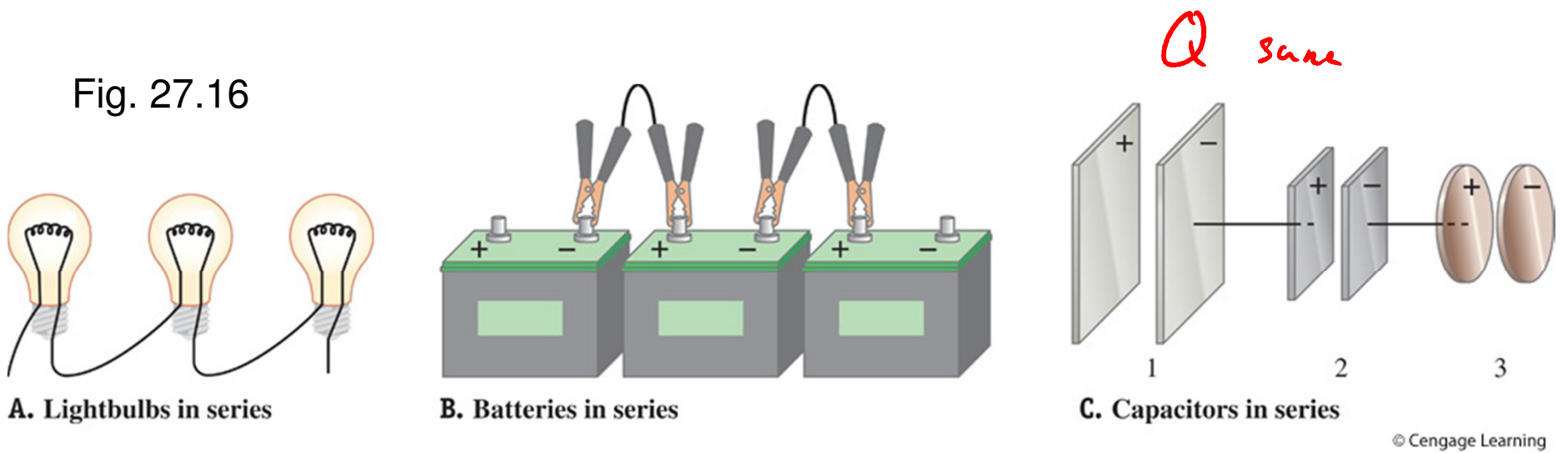


Fig. 27.21

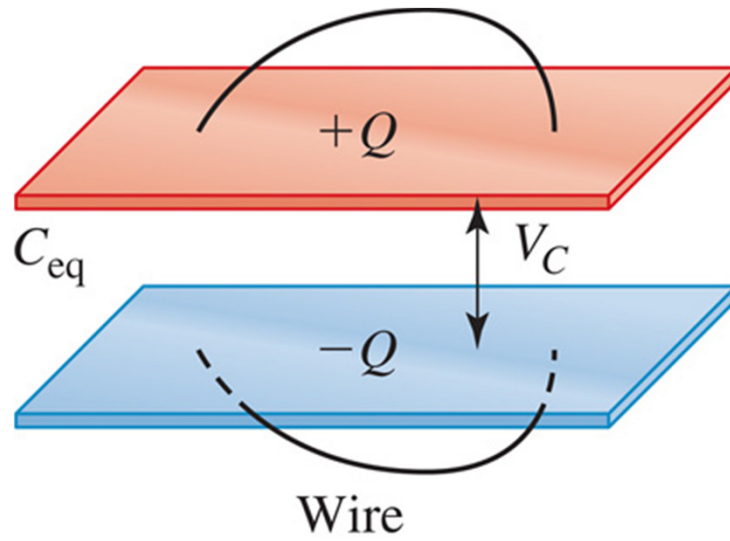


A.

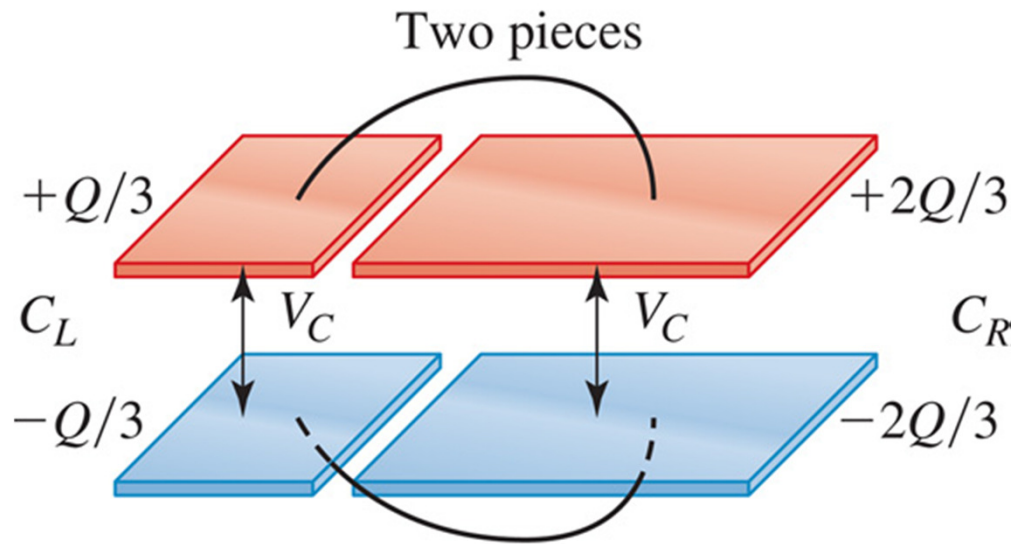

B.

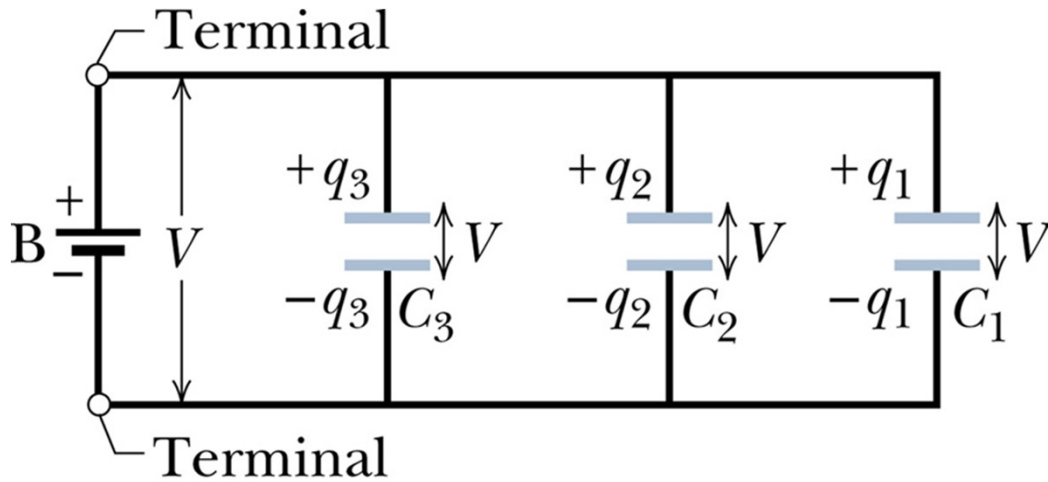What's the total C of this parallel set of caps?



$$q_1 = C_1 V \quad q_2 = C_2 V$$

$$q_3 = C_3 V$$





$$q_{tot} = q_1 + q_2 + q_3$$

$$q_{tot} = C_1 V + C_2 V + C_3 V$$


$$q_{tot} = V (C_1 + C_2 + C_3)$$

C_{tot}

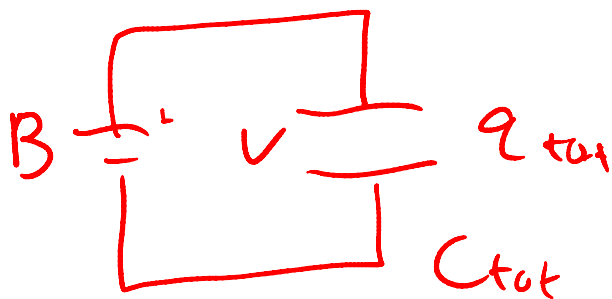

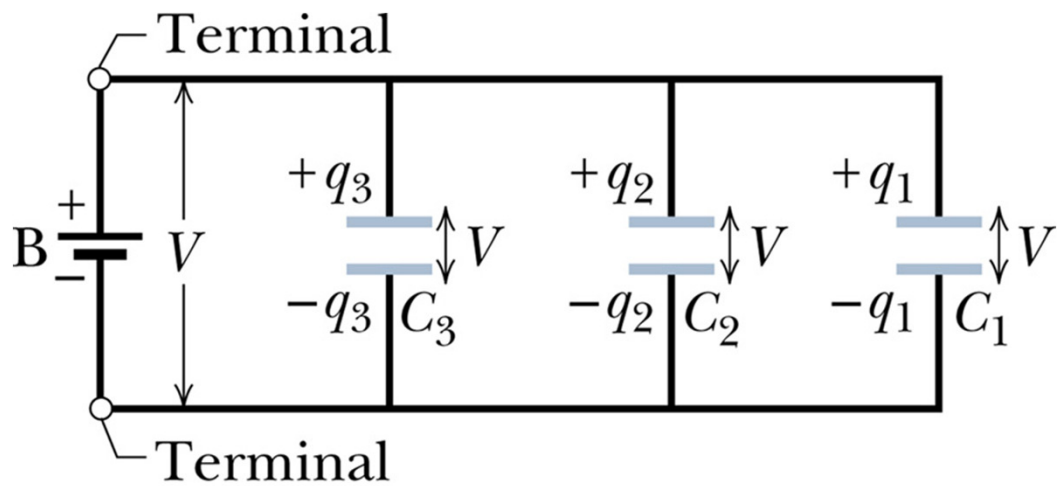

(a)

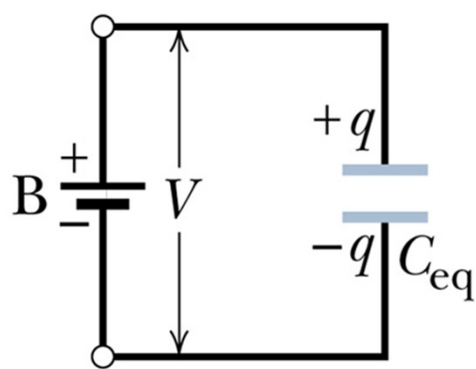


(b)


$$= C_{TOT} = C_1 + C_2 + C_3$$

$$C_{TOT} = \sum C_n$$


Fig. 27.15

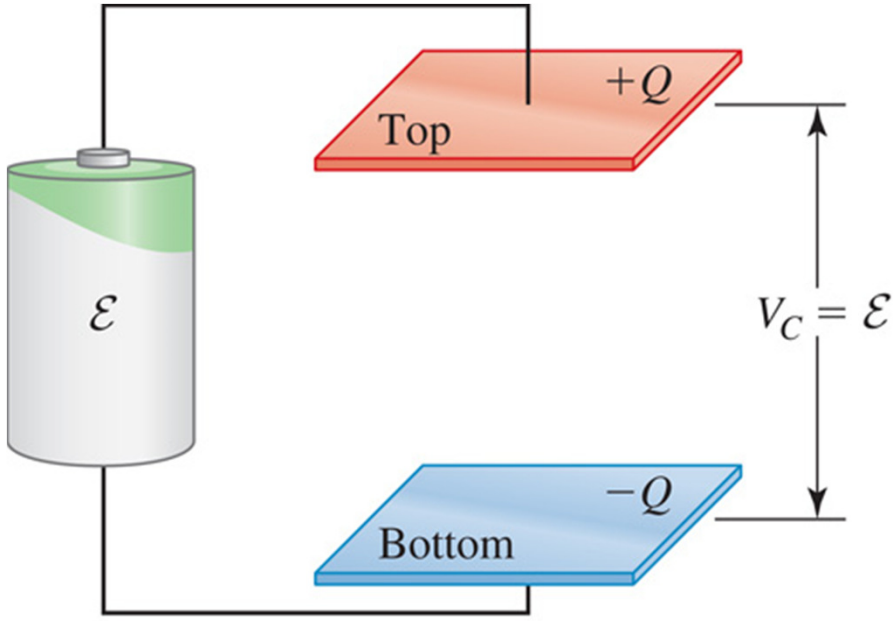

A.

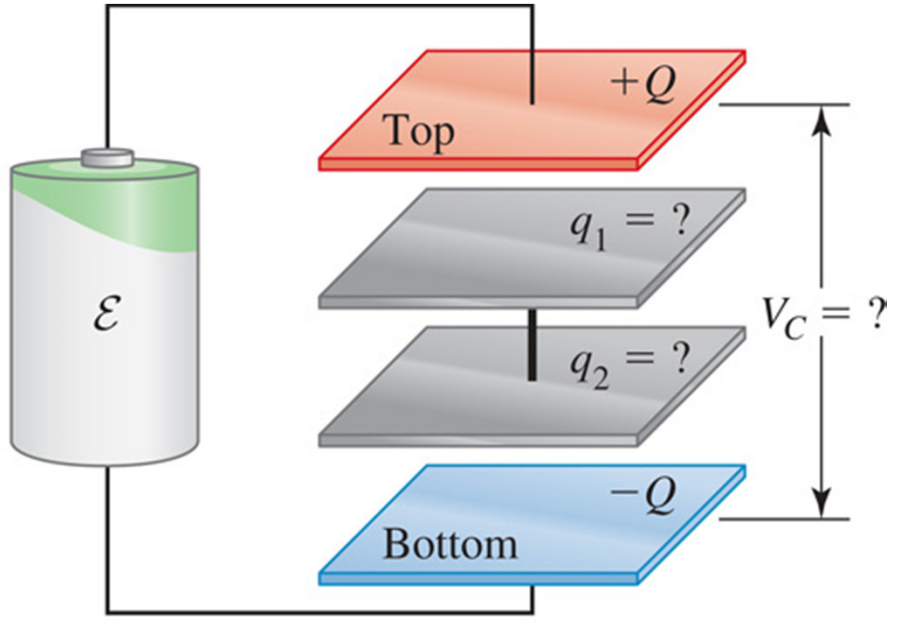


B.

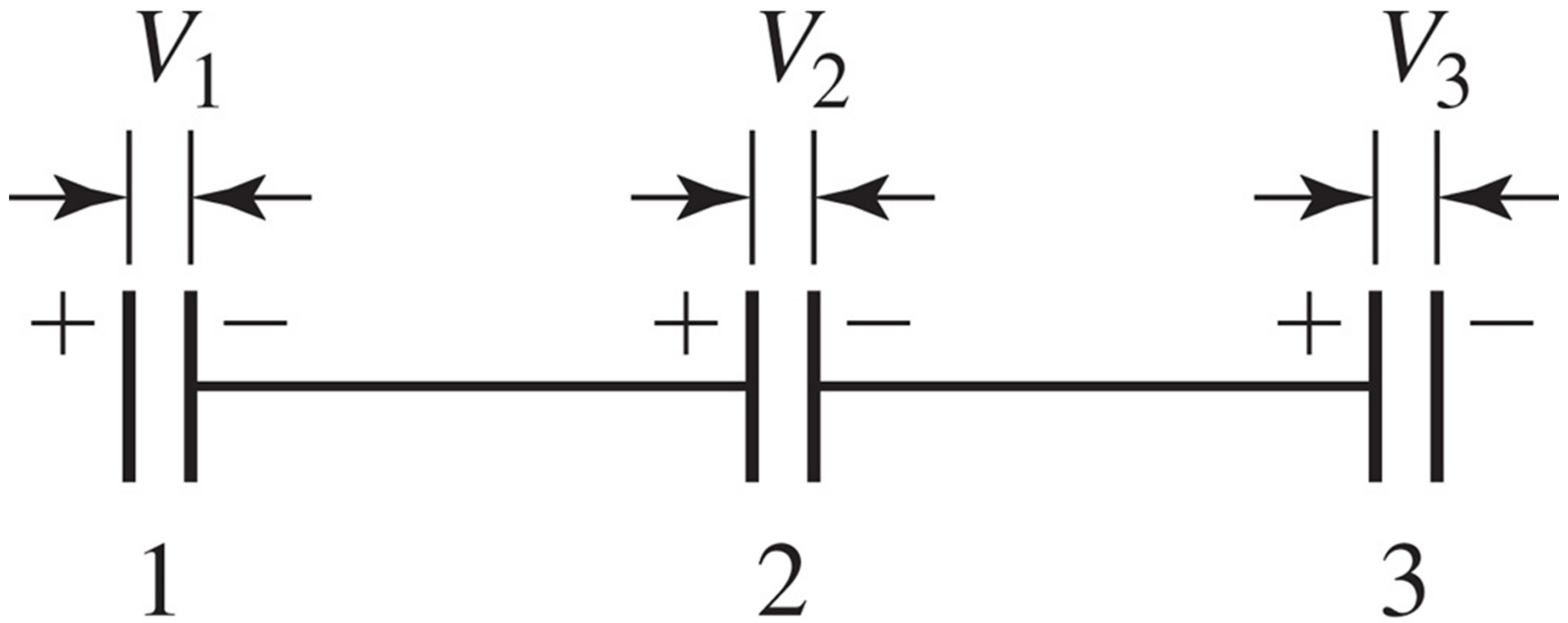

$$\leftarrow \Delta V = V_1 + V_2 + V_3 \rightarrow$$


Fig. 27.17

Fig. 27.19

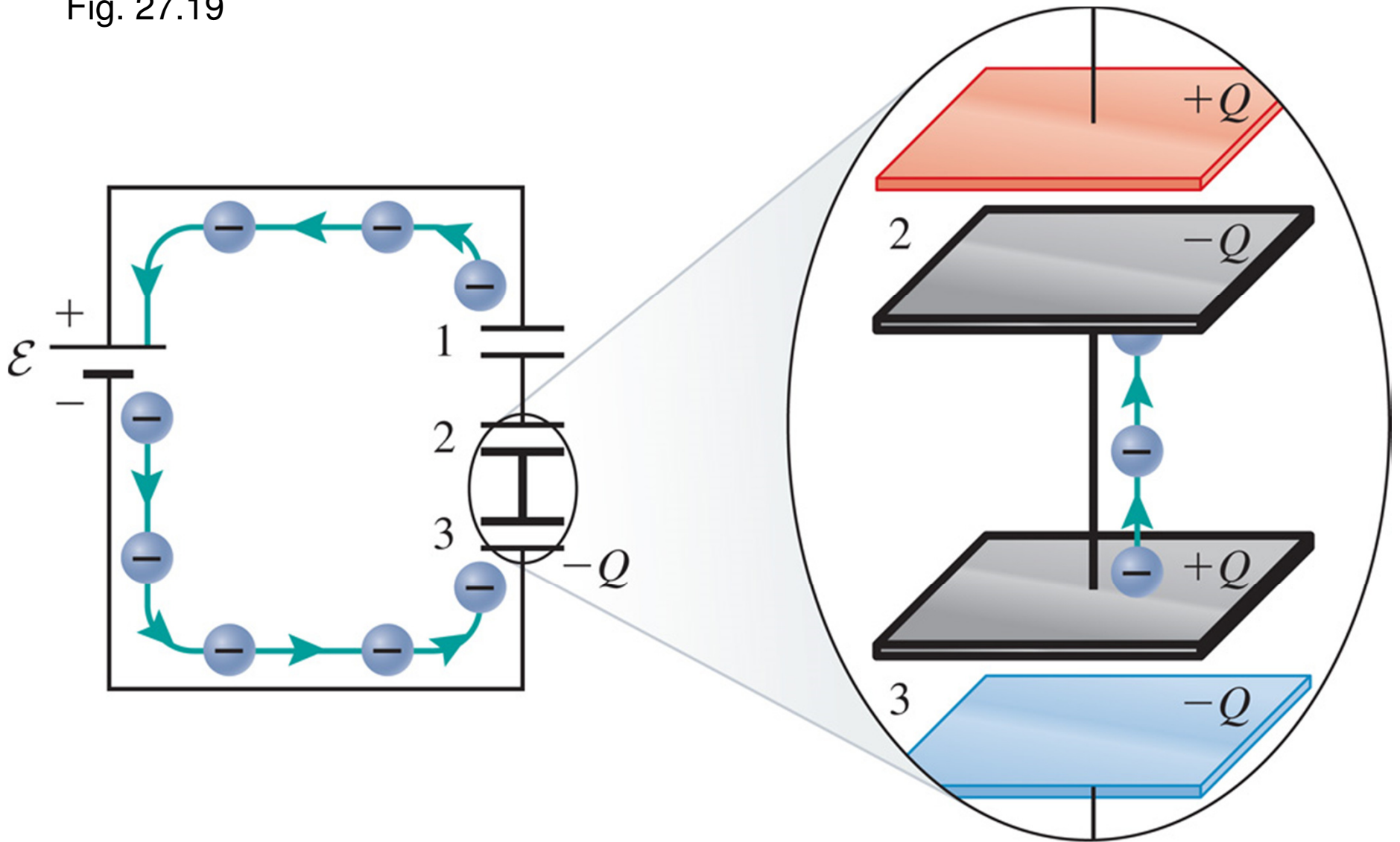


What's the total C of this series set of caps?
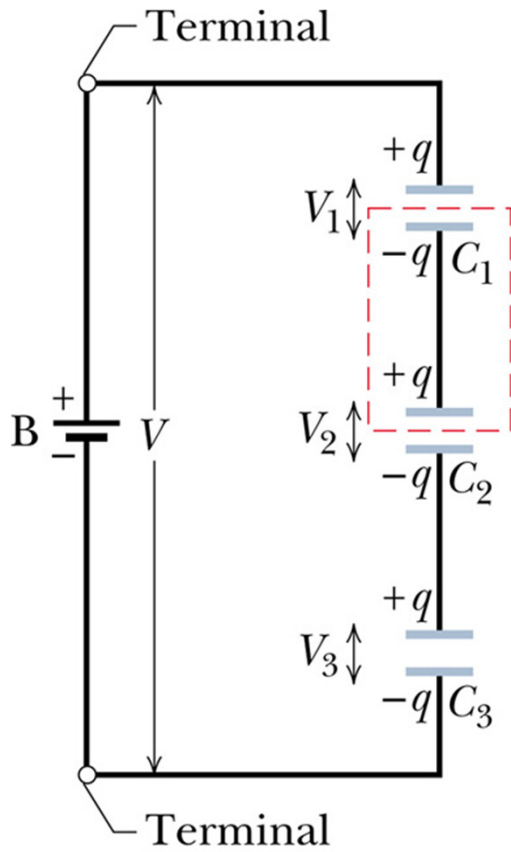
$$V_1 = \frac{q}{C_1} \quad V_2 = \frac{q}{C_2} \quad V_3 = \frac{q}{C_3}$$



(a)

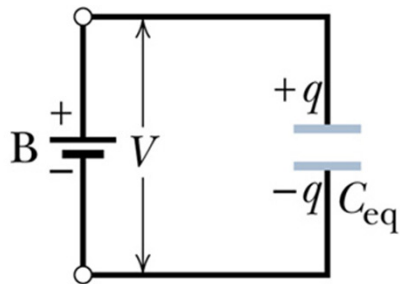


(b)

$$V = V_1 + V_2 + V_3$$


$$V = \left(\frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3} \right)$$

$$V = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$
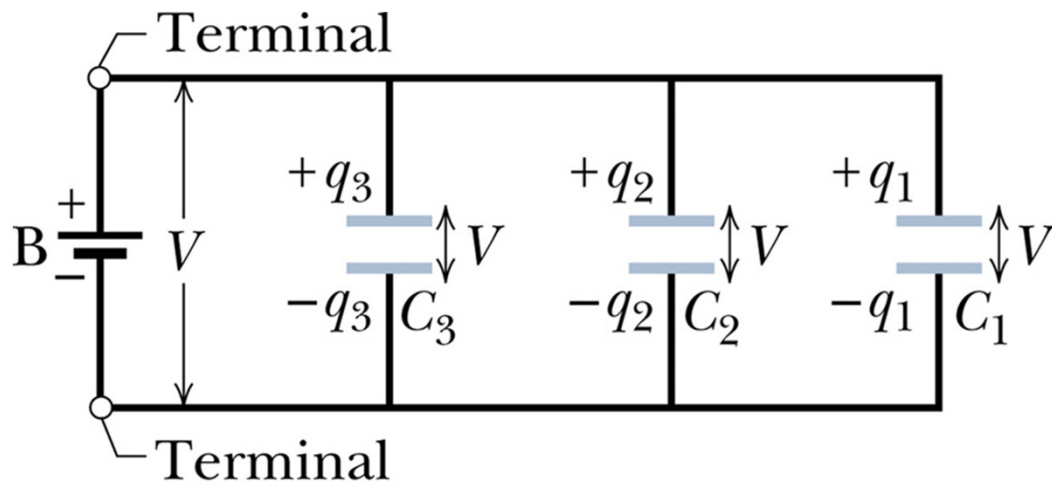
$$\text{Or: } \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$




parallel connection

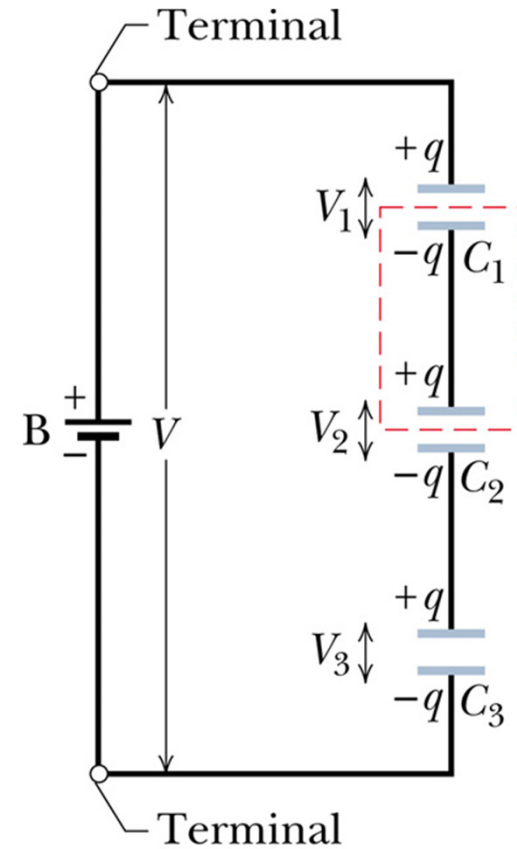

Series Connection


What are charges and voltages everywhere if we hook this up to a 12.5V car battery?

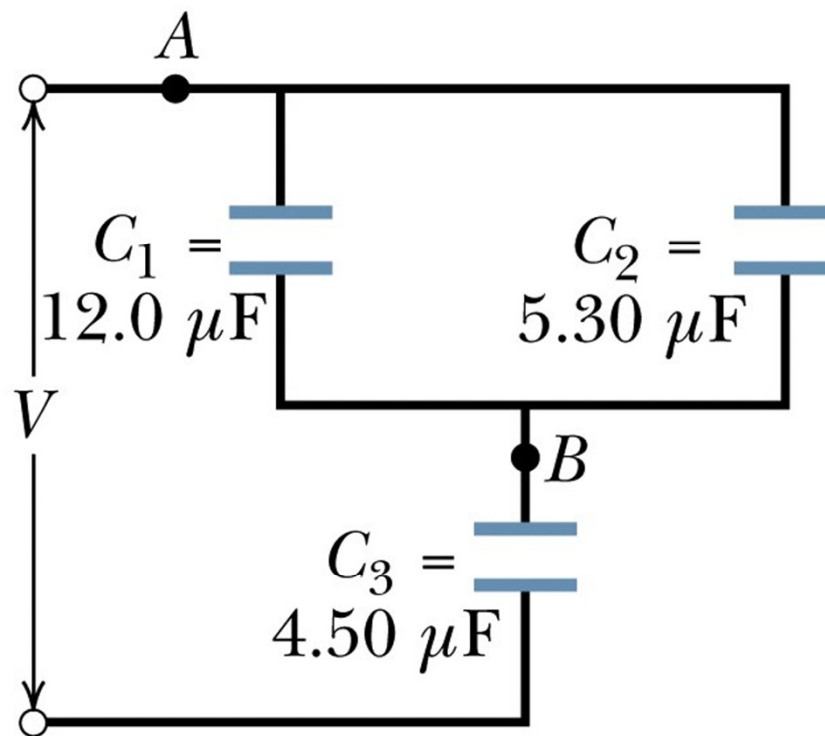We first reduce the circuit to a single capacitor.



(a)

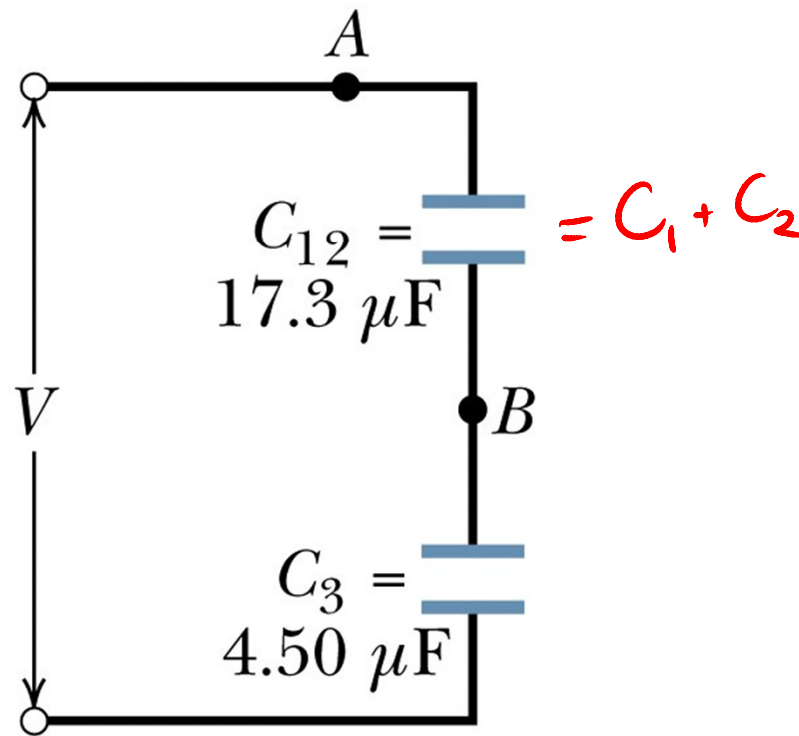
The equivalent of parallel capacitors is larger.



(b)


The equivalent of series capacitors is smaller.
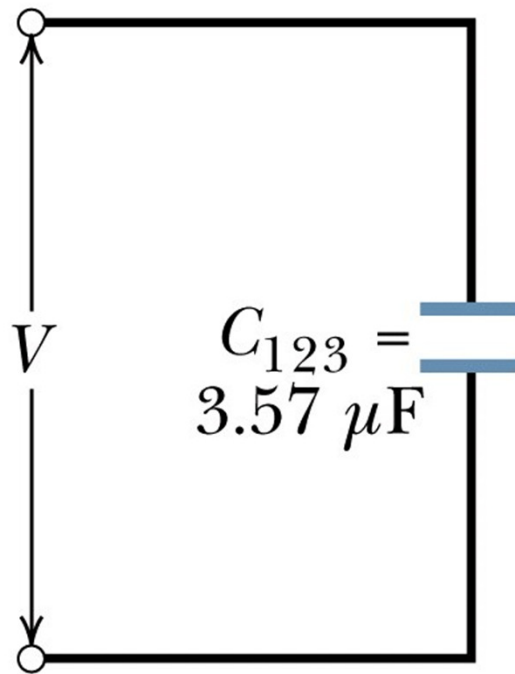
$$\frac{1}{C_{123}} = \frac{1}{C_{12}} + \frac{1}{C_3}$$




(c)

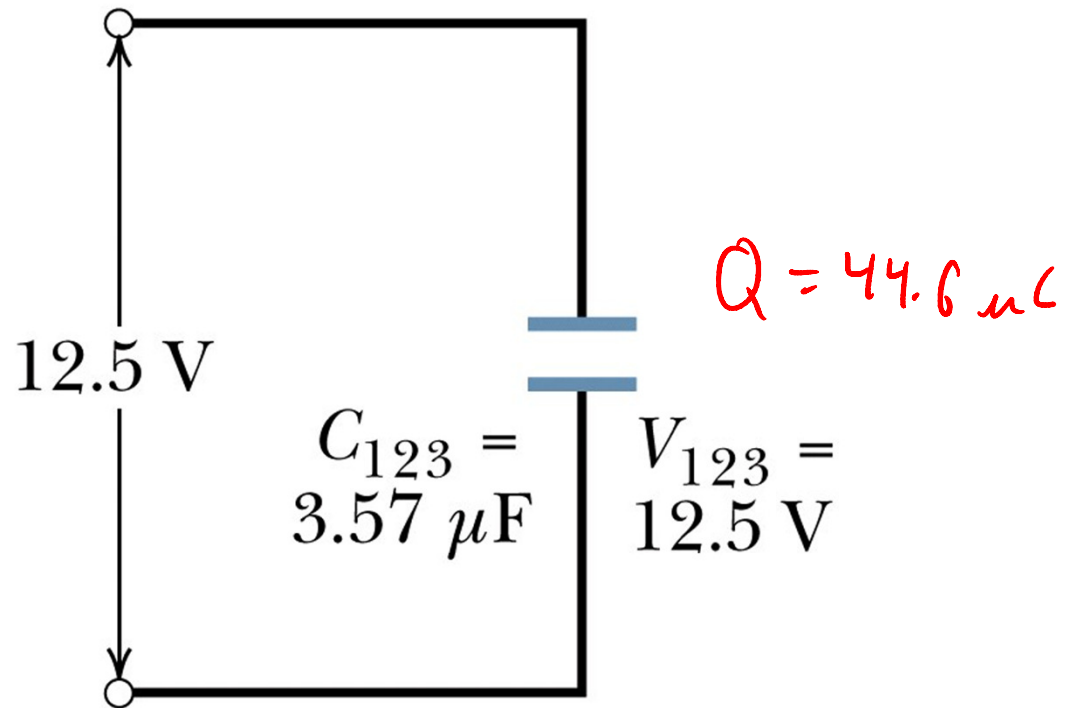Next, we work backwards to the desired capacitor.




(d)

Applying $q = CV$
yields the charge.

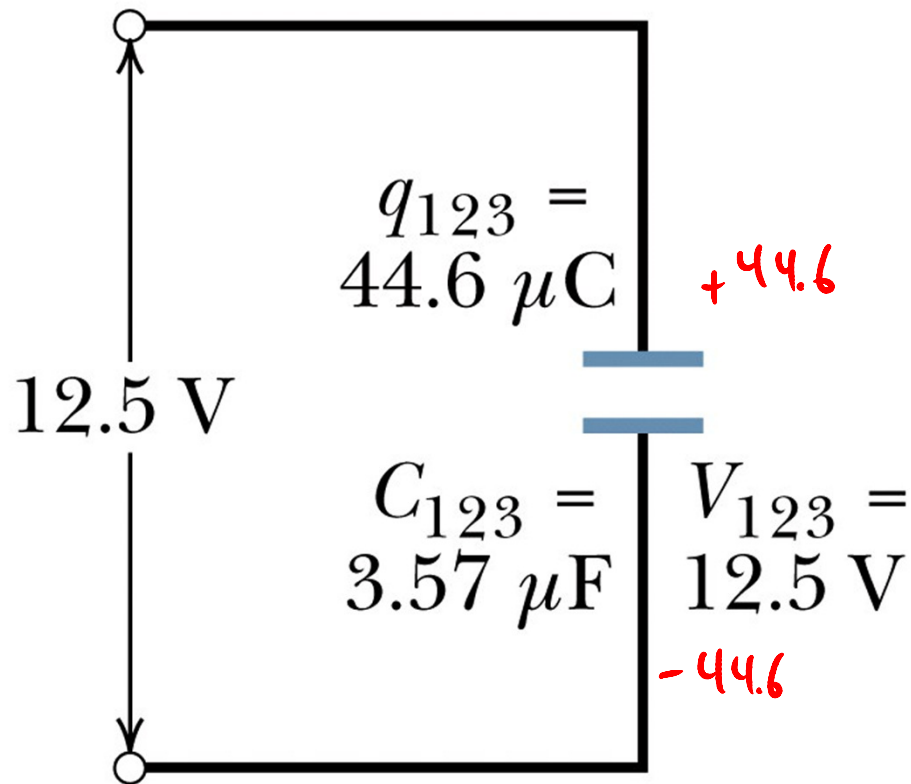


(e)

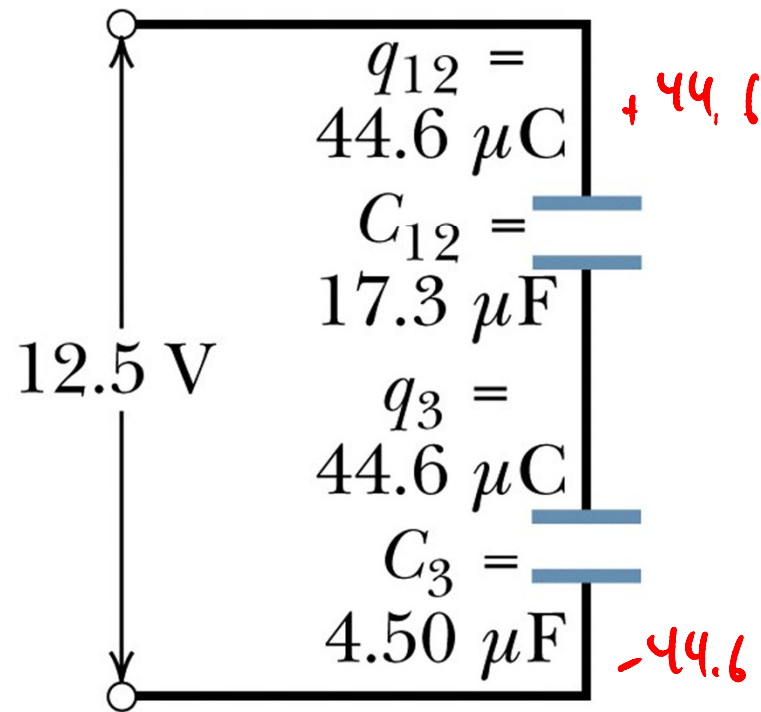Series capacitors and their equivalent have the same q (“seri- q ”).




(f)

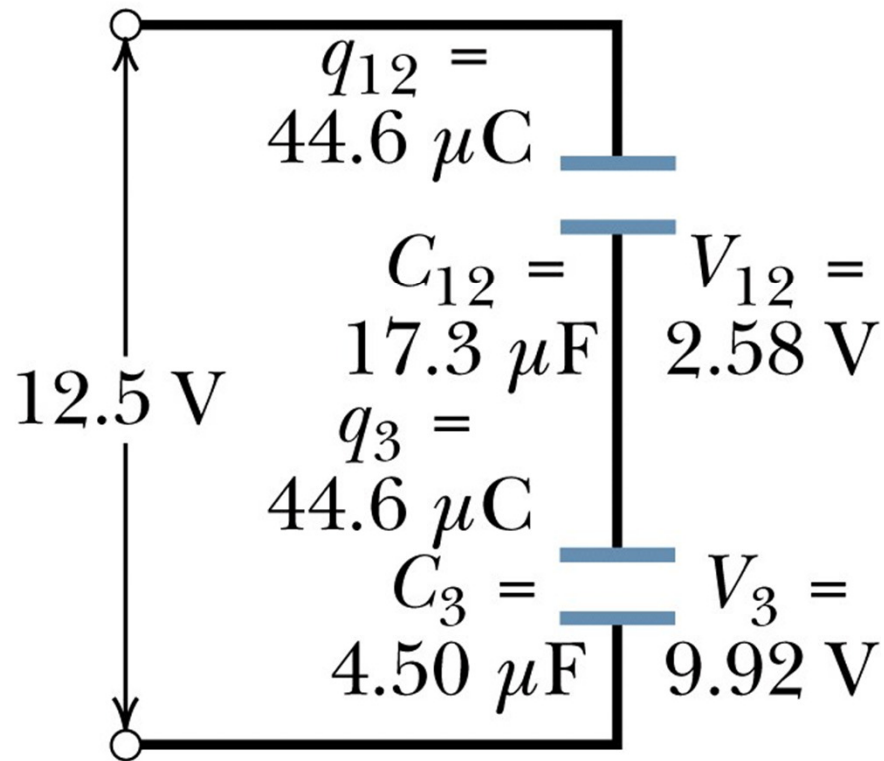Applying $V = q/C$ yields the potential difference.




(g)

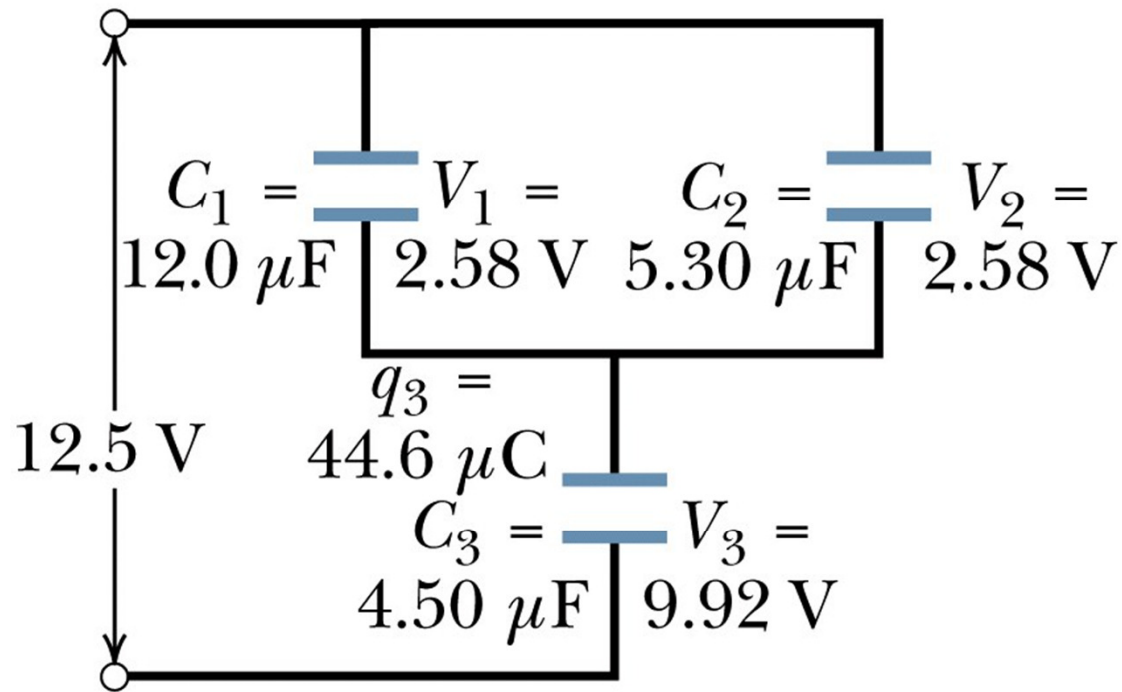Parallel capacitors and their equivalent have the same V (“par- V ”).



(h)

Applying $q = CV$
yields the charge.

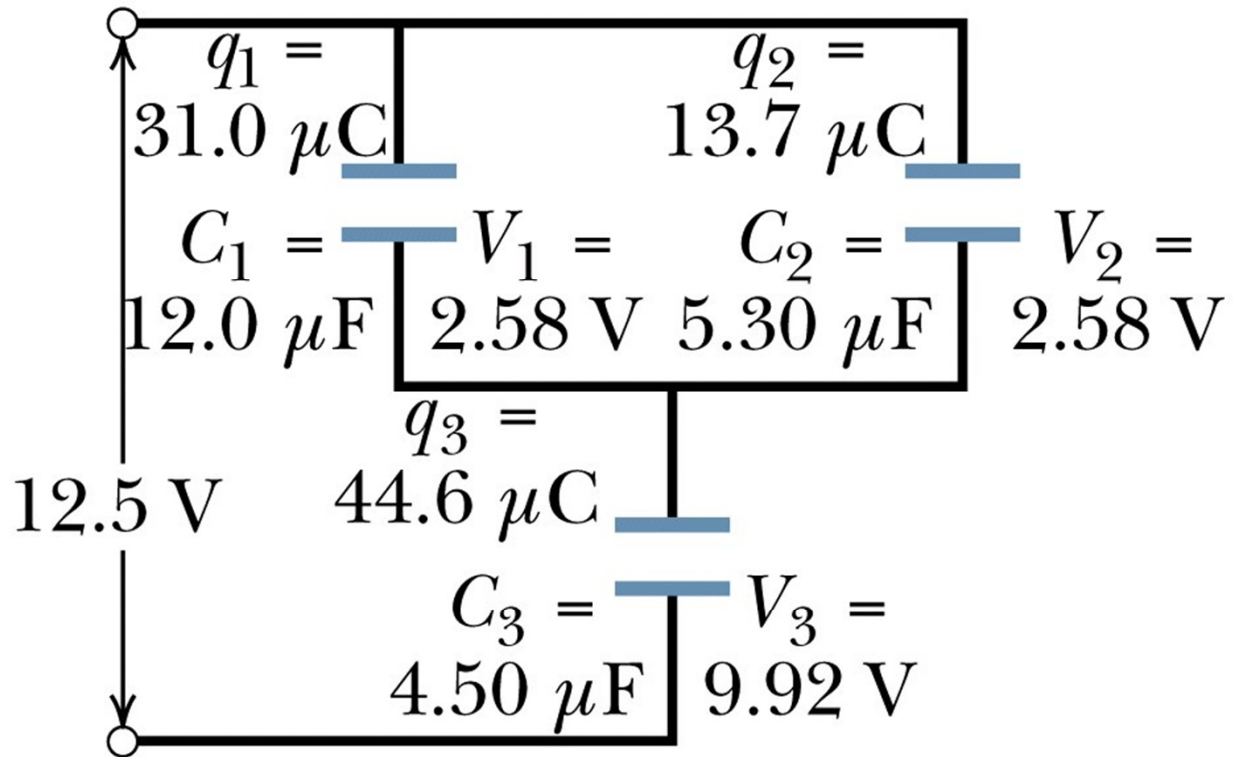


(i)

You work out this example:

A $2\ \mu\text{F}$ and a $4\ \mu\text{F}$ capacitor are connected in series with an 18V battery.

What are Q and V across each capacitor?

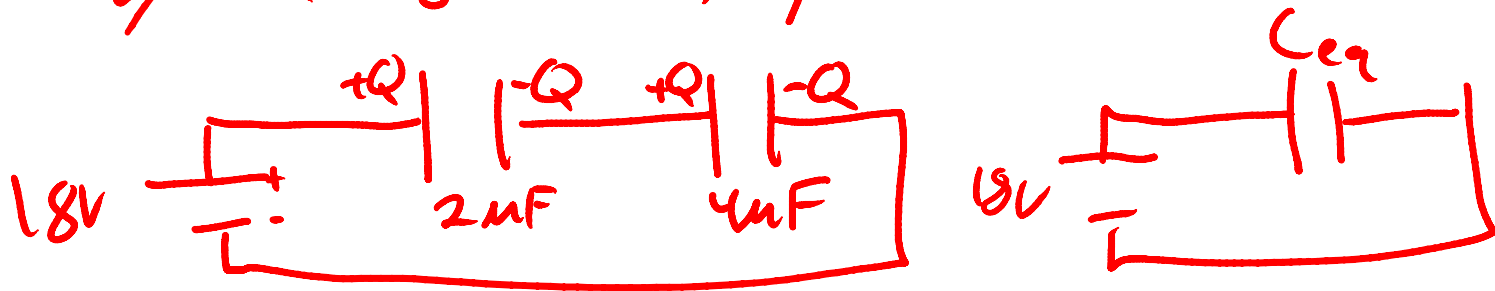a $2\mu\text{F}$ and a $4\mu\text{F}$ cap connected in series w/ an 18V battery. What are $Q + V$ on each?



in series. $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{2\mu\text{F}} + \frac{1}{4\mu\text{F}}$

$$C_{eq} = \frac{4}{3} \mu\text{F} \quad V = 18\text{V} \quad Q = CV = \left(\frac{4}{3}\mu\text{F}\right)(18) = 24\mu\text{C}$$


$$Q_1 = C_1 V \quad Q_2 = C_2 V$$



$$V_1 = \frac{Q}{C_1} = \frac{24\mu\text{C}}{2\mu\text{F}} = 12\text{V} \quad V_2 = \frac{Q}{C_2} = \frac{24\mu\text{C}}{4\mu\text{F}} = 6\text{V}$$

$$12\text{V} + 6\text{V} = 18\text{V} \checkmark$$

Now take those same capacitors, unplug them from the battery carefully so as not to lose their charge, and connect them together in parallel instead.

What are Q and V across each capacitor?

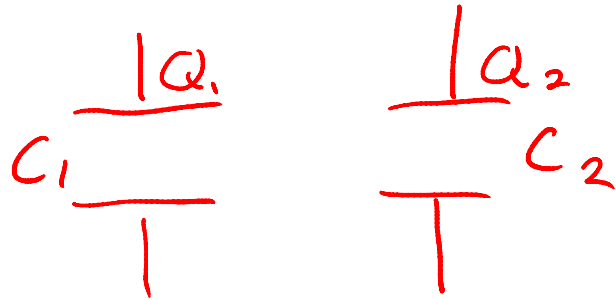

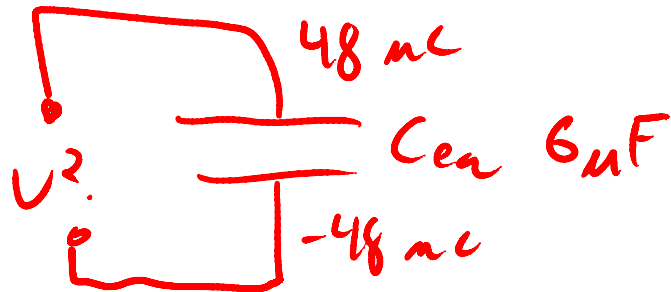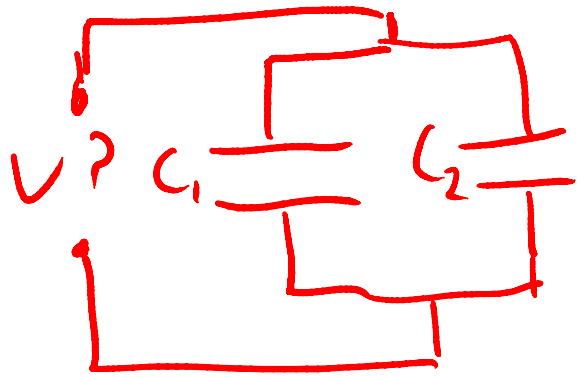

24 μC on each before un plugged
 so 48 μC total

C's in || $C_{eq} = C_1 + C_2 = 6 \mu\text{F}$

$$V = \frac{Q}{C_{eq}} = \frac{48 \mu\text{C}}{6 \mu\text{F}} = 8\text{V}$$

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$= 2 \mu\text{F} \cdot 8\text{V}$$

$$= 4 \mu\text{F} \cdot 8\text{V}$$

$$Q_1 = 16 \mu\text{C}$$

$$Q_2 = 32 \mu\text{C}$$

$$Q_{\text{TOT}} = 48 \mu\text{C} = 16 + 32$$

Do Equivalent Capacitance Handout