

Kirchoff's Rules: Loop Sum.

$$\textcircled{1} \quad I_1 + I_3 = I_2$$

(b a d b)


KVL: CCW over left loop (1)


$$\textcircled{2} \quad +\mathcal{E}_1 - I_1 R_1 + I_3 R_3 = 0$$

(b d c b)

KVL: CCW over right loop (2)
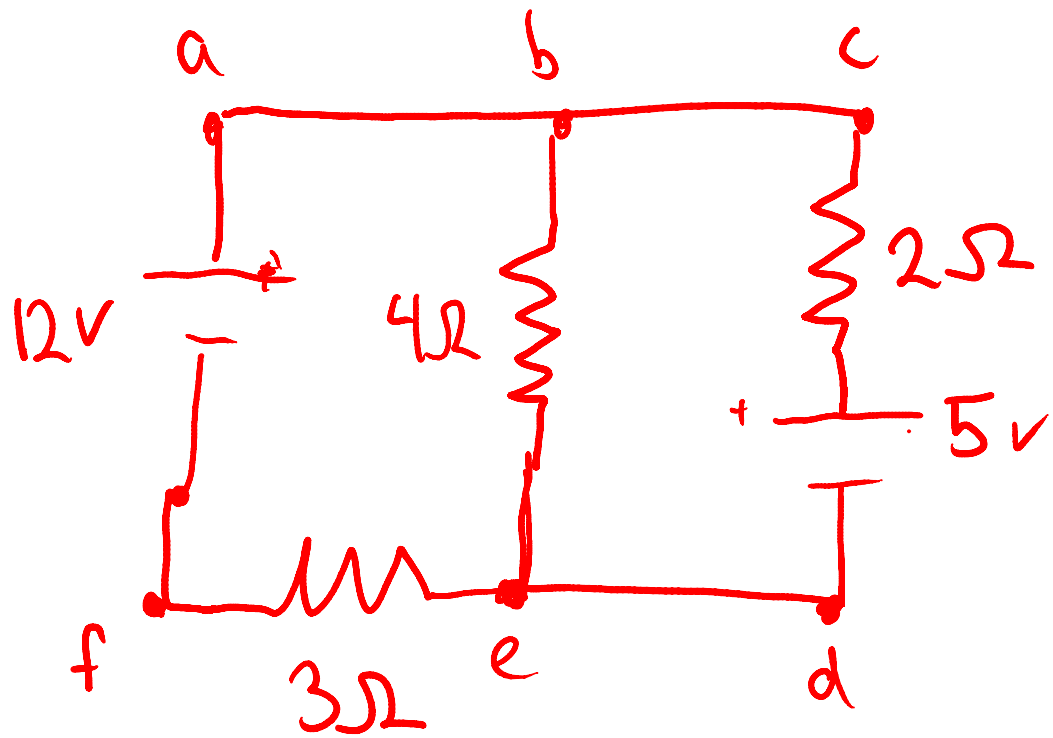
$$\textcircled{3} \quad -I_3 R_3 - I_2 R_2 - \mathcal{E}_2 = 0$$



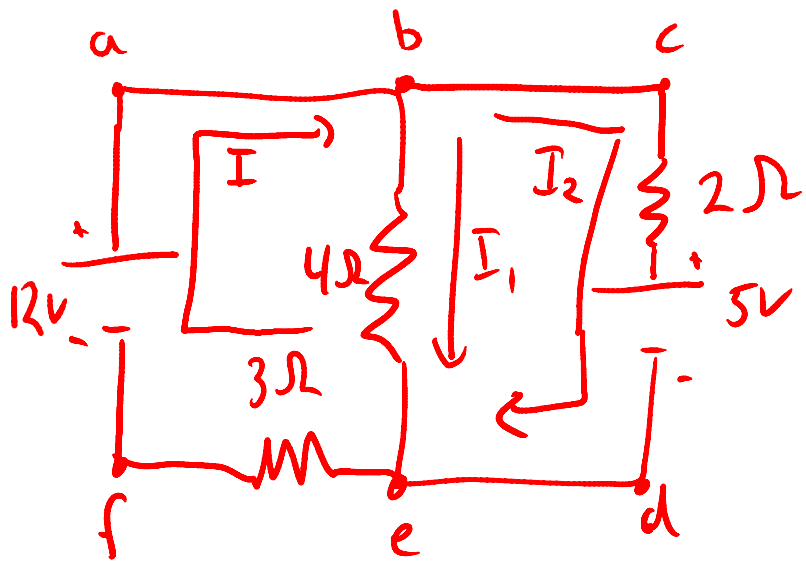

KJA: @ b $I = I_1 + I_2$ (1)

KLR: around CW [fabcdef]

$$+12V - I_2 2\Omega - 5V - I 3\Omega = 0 \quad (2)$$

CW [fabe f]

$$+12V - I_1 4\Omega - I (3\Omega) = 0 \quad (3)$$

Subst (1) into (2), (3)

$$(2) \quad 12V - 2\Omega I_2 - 5V - 3\Omega(I_1 + I_2) = 0 = 7V - 3\Omega I_1 - 5\Omega I_2 = 0$$

$$(3) \quad 12V - 4\Omega I_1 - 3\Omega(I_1 + I_2) = 0 = 12V - 7\Omega I_1 - 3\Omega I_2 = 0$$

divide all by 1Ω

$$(2) \quad 7A - 3I_1 - 5I_2 = 0$$

$$(3) \quad 12A - 7I_1 - 3I_2 = 0$$

solve (3) for $I_2 = \frac{12A - 7I_1}{3} = 4A - \frac{7}{3}I_1$

Subst into ②


$$0 = 7A - 3I_1 - 5\left(4A - \frac{7}{3}I_1\right)$$


$$\text{solve for } I_1 = 1.5A$$

$$\text{so } I_2 = \frac{12A - 7(1.5A)}{3} = 0.5A$$

$$I = I_1 + I_2 = 2A$$

Ideal vs. real meters

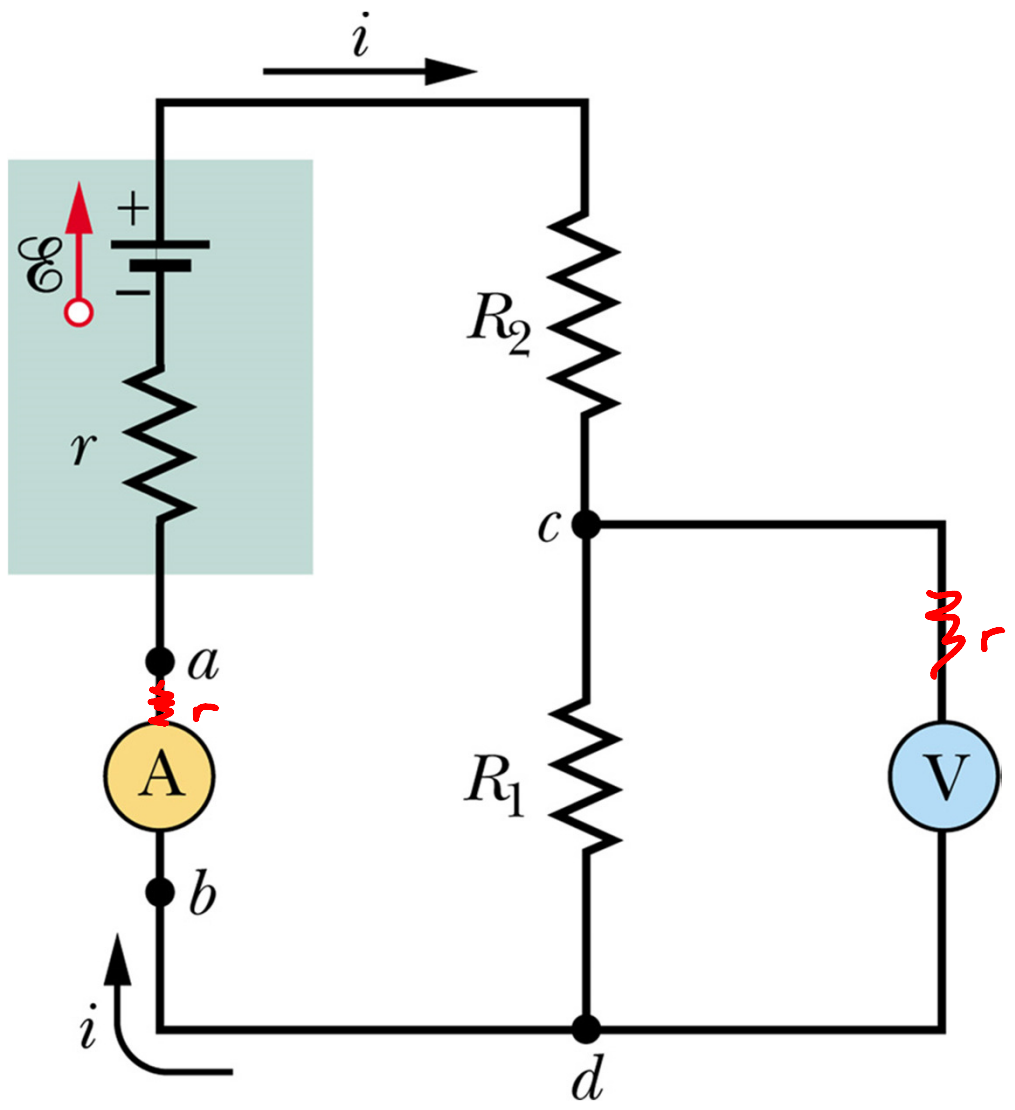

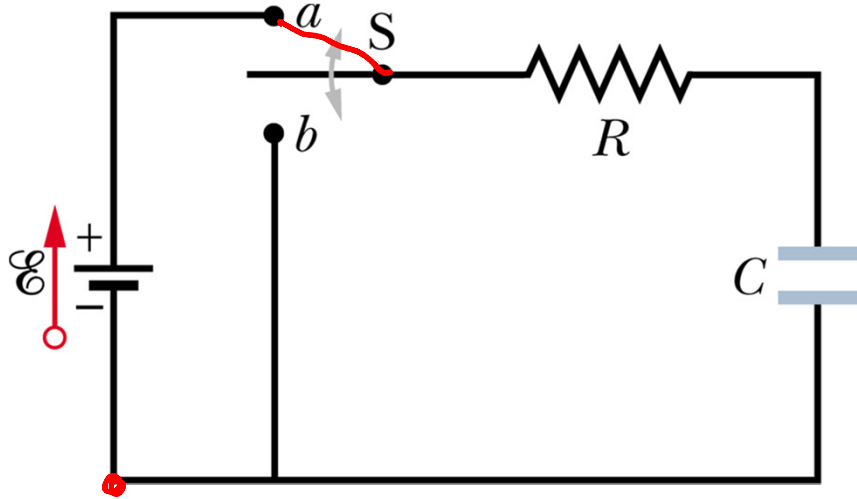

$$q = 0 \text{ @ } t = 0$$


$$V_c = \frac{q}{C}$$

$$\text{KLR: } +\varepsilon - IR - \frac{q}{C} = 0$$

$$\varepsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

$$R \frac{dq}{dt} + \frac{q}{C} = \varepsilon$$
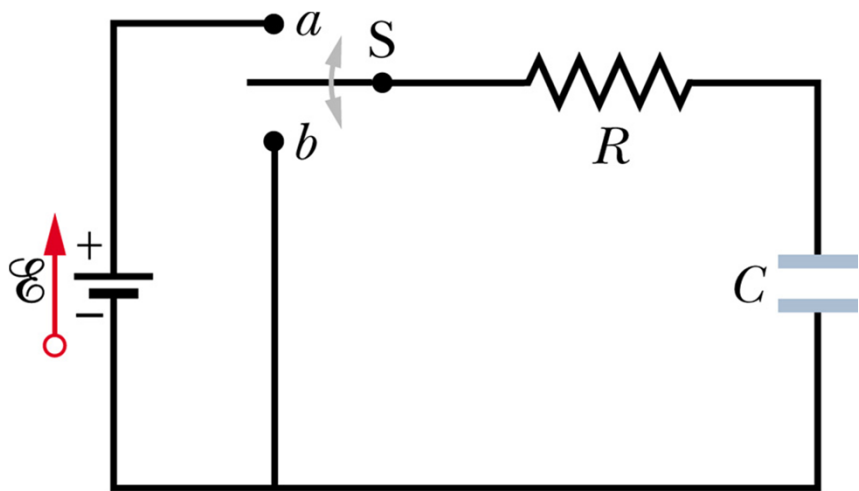
$$\frac{dq}{dt} + \frac{q}{RC} = \frac{\varepsilon}{R}$$



$$\frac{dq}{dt} + \frac{q}{RC} = \frac{\mathcal{E}}{R}$$

Soln: $q(t) = q_{\text{Final}} + K e^{-\alpha t}$

q_{Final} : @ $t \rightarrow \infty$ $V_C = \mathcal{E}$


$$q(\infty) = q_{\text{final}} + e^{-\infty} K$$


$$0 + \frac{q_f}{RC} = \frac{\mathcal{E}}{R} \Rightarrow q_f = C\mathcal{E}$$


@ $t=0, q=0$ $q(0) = 0 = q_f + K e^{-\alpha \cdot 0}$ so $K = -C\mathcal{E}$


$$q(t) = C\mathcal{E} - C\mathcal{E} e^{-t/RC}$$

$$q(t) = C\mathcal{E} (1 - e^{-t/RC})$$

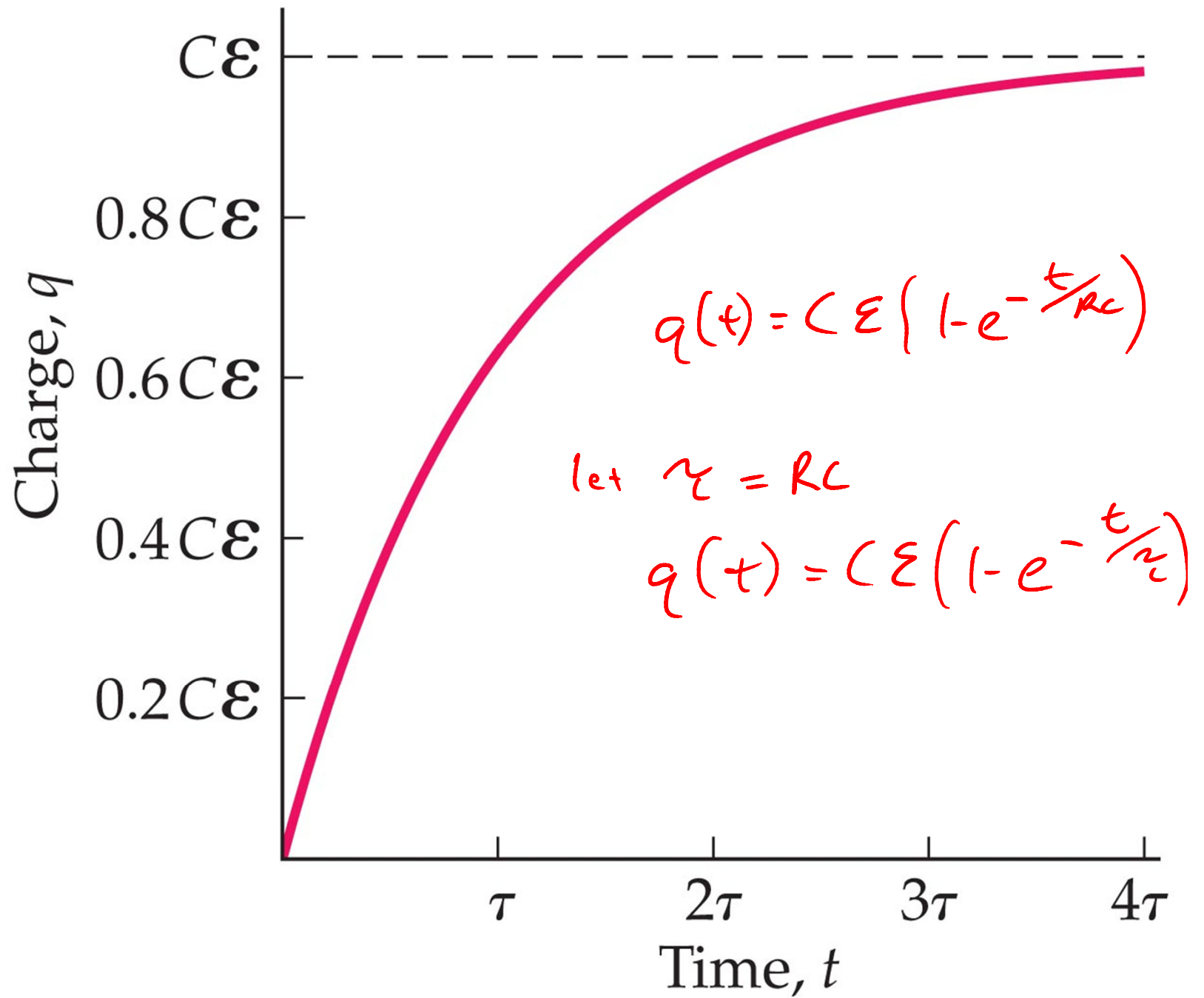


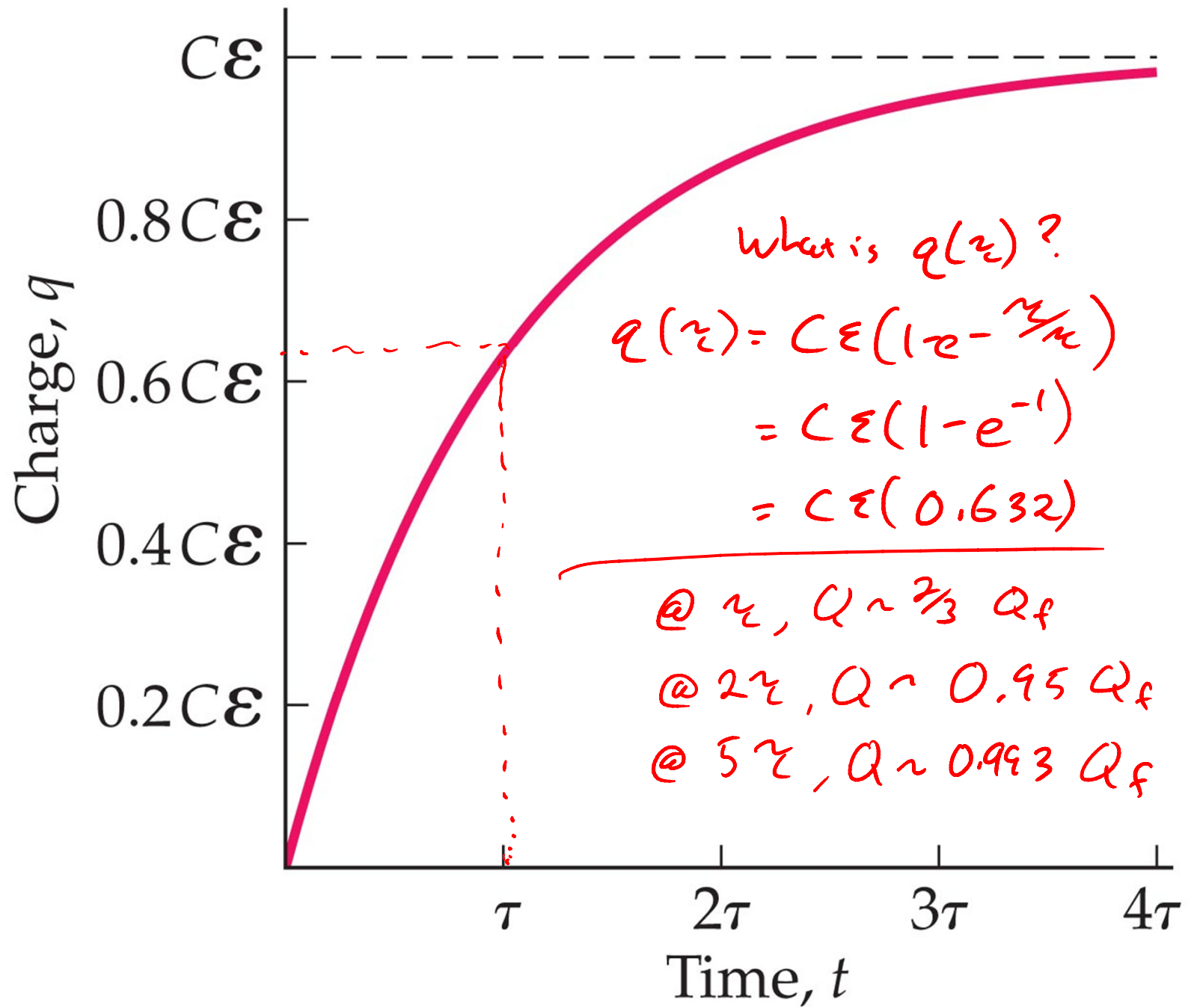

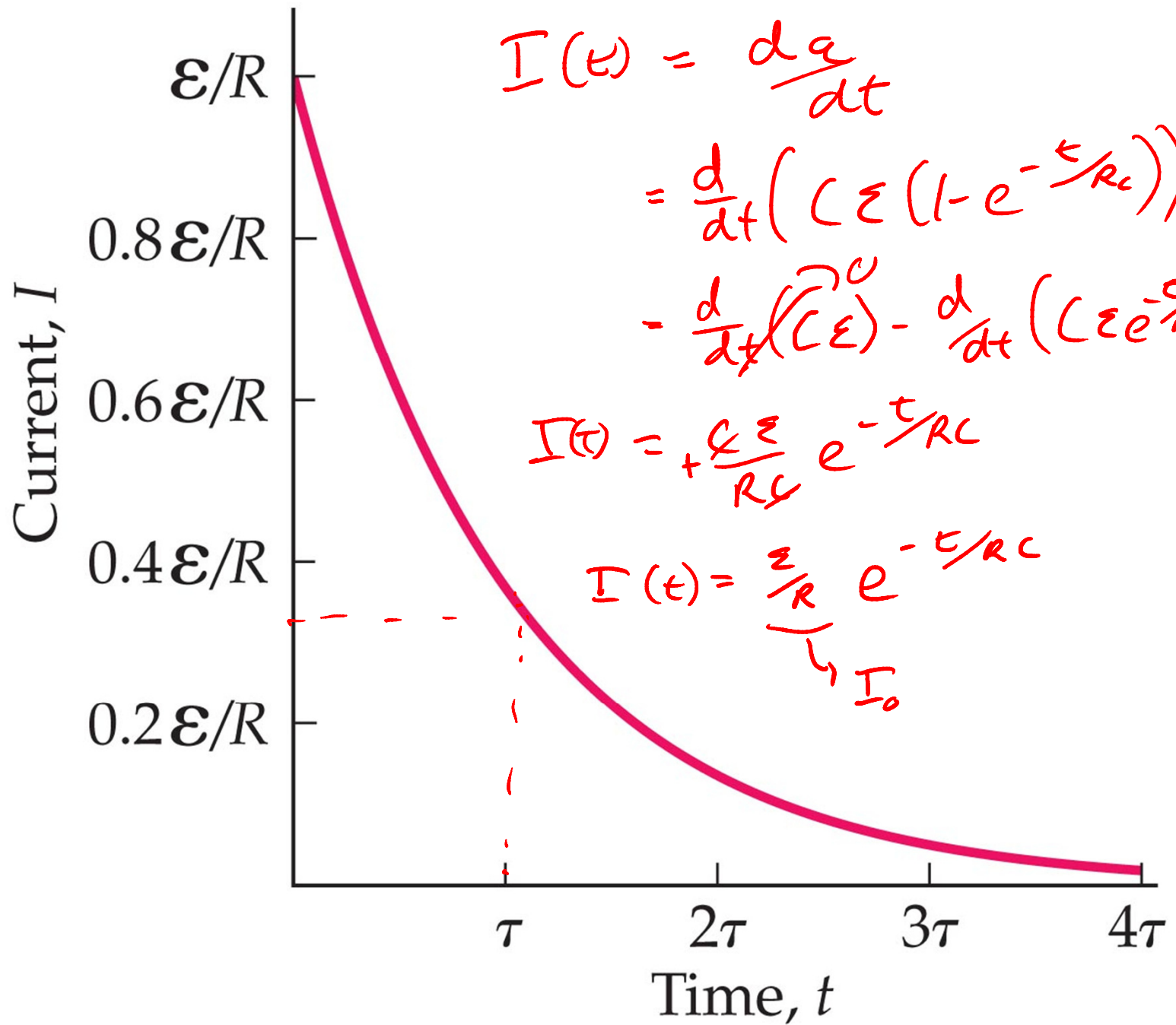

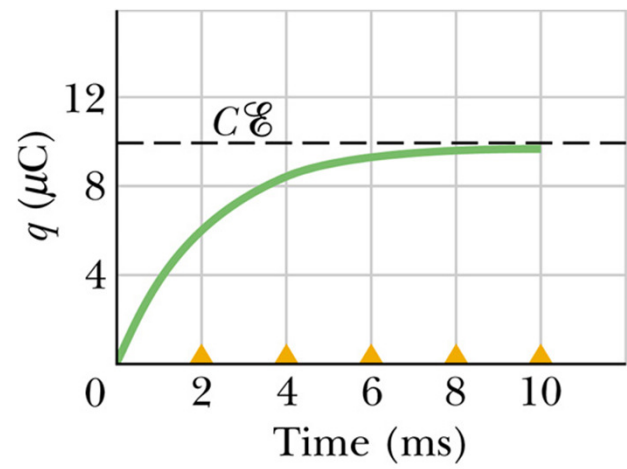


(a)

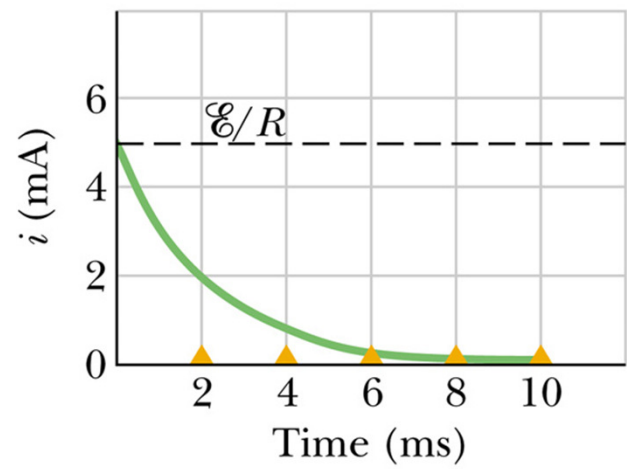

(b)

Charging example:

a) What is initial current?

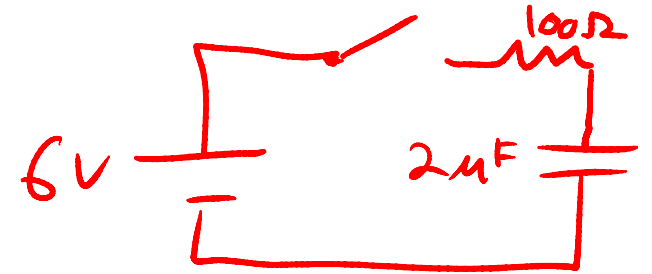


Charging example:

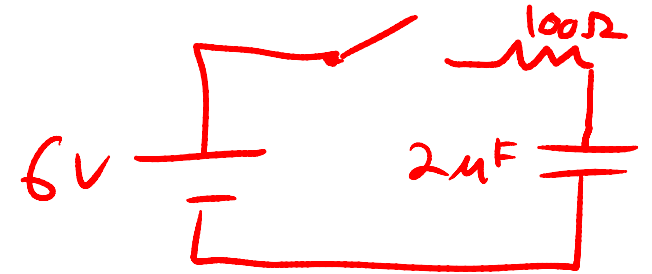a) What is initial current?


$$I(t) = \frac{\epsilon}{R} e^{-t/\tau}$$

$$I(0) = \frac{\epsilon}{R} e^{-0/\tau} = \frac{\epsilon}{R} = \frac{6V}{100\Omega} = 0.06A$$




Charging example:

b) What is final charge?

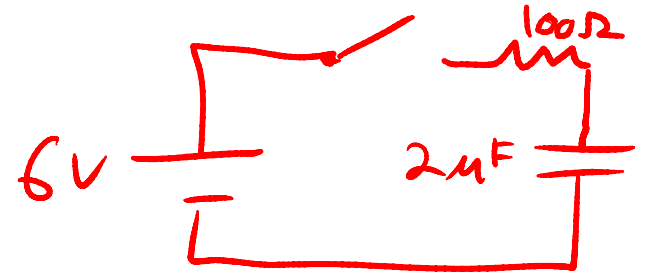

Charging example:


b) What is final charge?

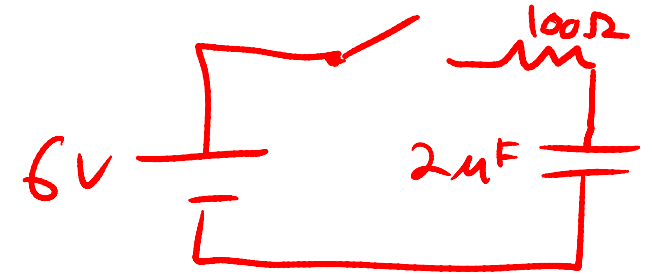


$$q(t) = C \varepsilon (1 - e^{-t/\tau})$$
$$q(\infty) = C \varepsilon (1 - e^{-\infty}) = C \varepsilon = (2 \times 10^{-6} \text{ F})(6 \text{ V}) = 12 \mu\text{C}$$

Charging example:

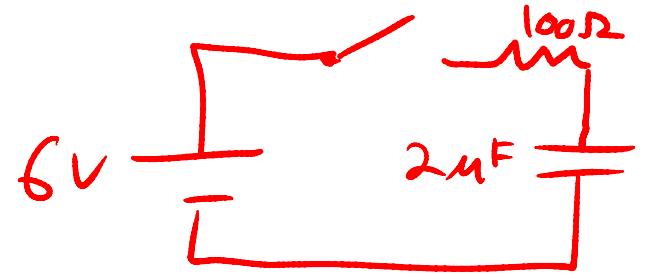c) How long to get to 90% of full charge?



Charging example:

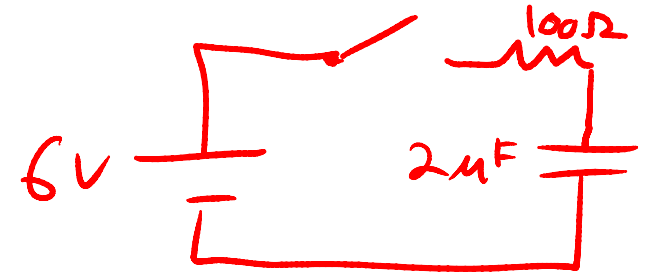

c) How long to get to 90% of full charge?

$$q(t) = C\varepsilon (1 - e^{-t/\tau})$$

$$Q_F = C\varepsilon$$

$$0.9 Q_F = 0.9 (C\varepsilon) = C\varepsilon (1 - e^{-t/\tau})$$

$$0.9 = 1 - e^{-t/\tau}$$

$$-0.1 = -e^{-t/\tau}$$


$$0.1 = e^{-t/\tau}$$

$$\ln(0.1) = -t/\tau$$


$$t = \tau \ln(0.1) = RC \ln(0.1)$$

$$= \ln(0.1) (100\Omega) (2 \times 10^{-6}\text{F}) = 460\mu\text{s}$$

Discharging a capacitor

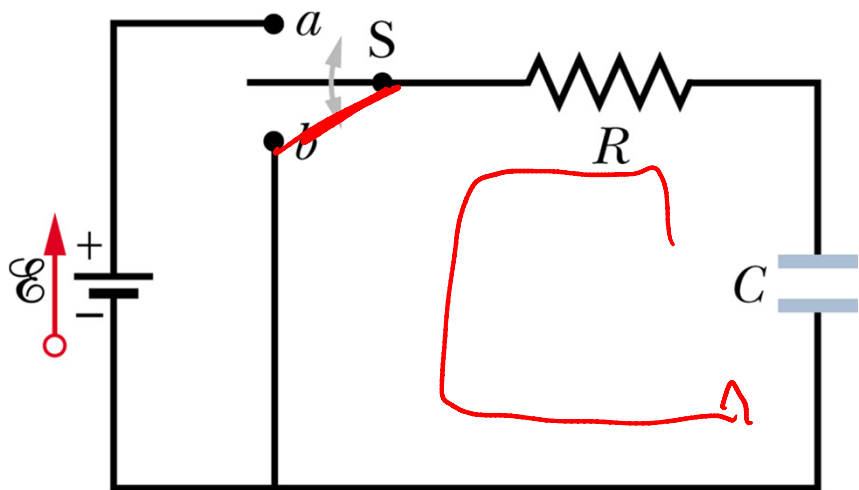

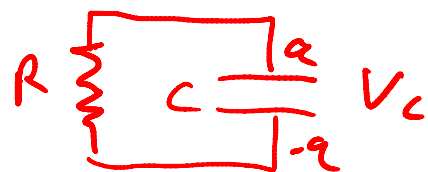Charged up to q , has V_c
move switch to b



$$I = V_c / R \quad q = CV_c$$


$$\text{Loop rule: } -IR - \frac{q}{C} = 0$$

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$q(t) = q_0 e^{-t/RC}$$

$$q_0 = CV_0 = \text{initial charge}$$


Current?

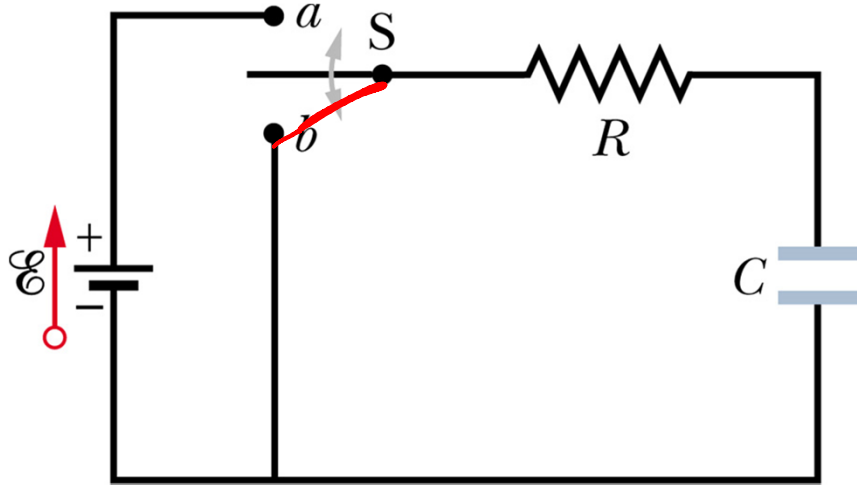

$$I = \frac{dq}{dt} = \frac{d}{dt} (q_0 e^{-t/\tau})$$


$$I(t) = - \frac{q_0}{RC} e^{-t/RC}$$

$\hookrightarrow I_0$

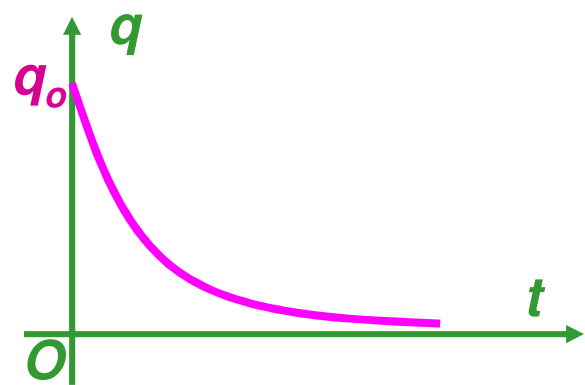

Discharging example:


a) What is initial charge?

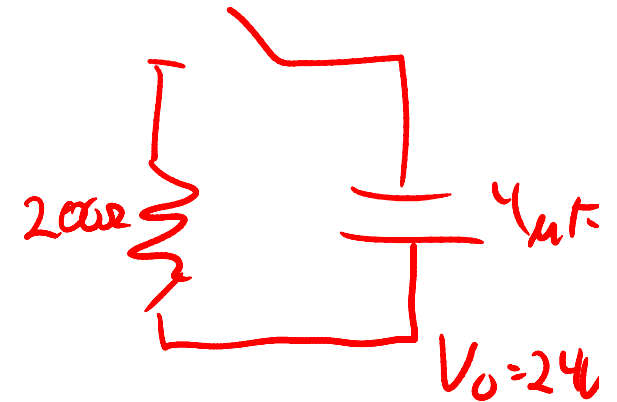

Discharging example:

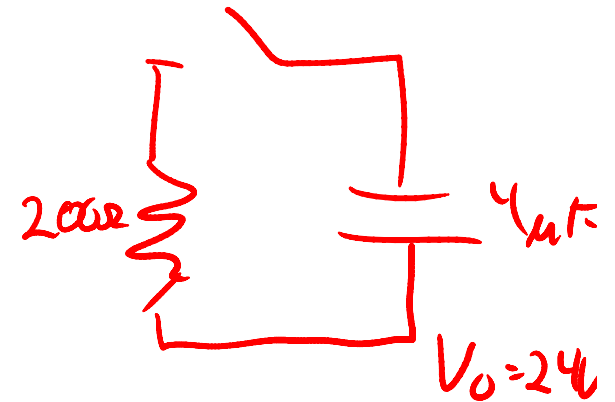
a) What is initial charge?

$$Q = CV = (4 \times 10^{-6} \text{ F})(24 \text{ V}) \\ = 96 \mu\text{C}$$



Discharging example:


b) What is initial current?

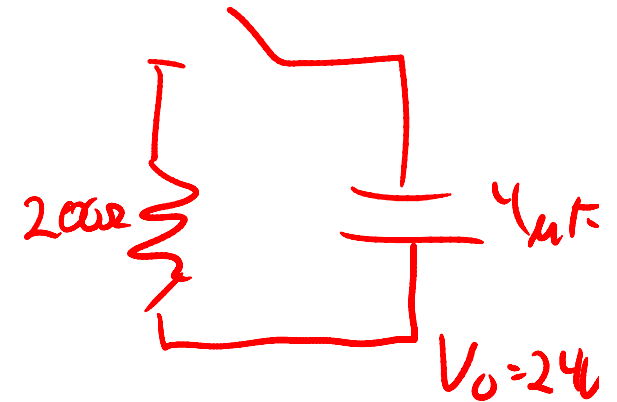

Discharging example:

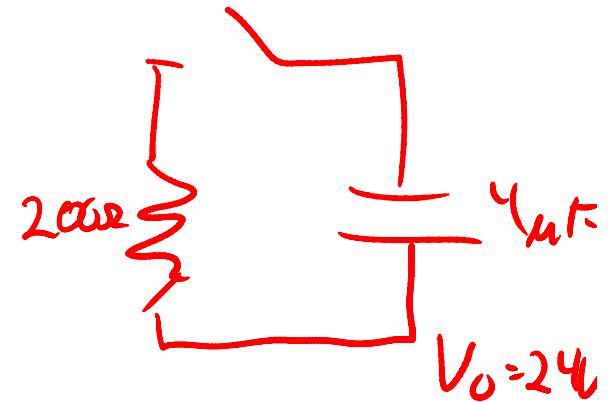
b) What is initial current?

$$I_0 = V_0 / R = \frac{24V}{200\Omega} = 0.12A$$



Discharging example:


c) What is time constant?

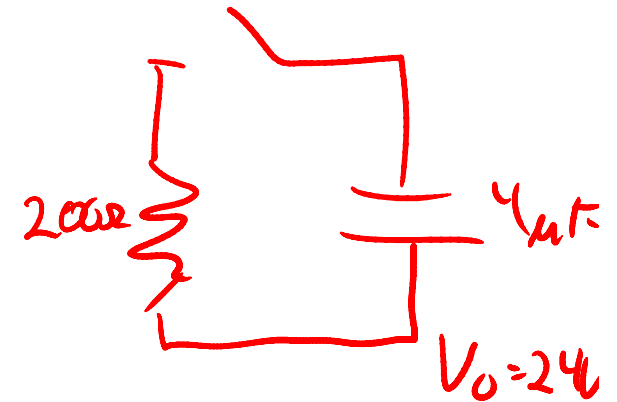

Discharging example:

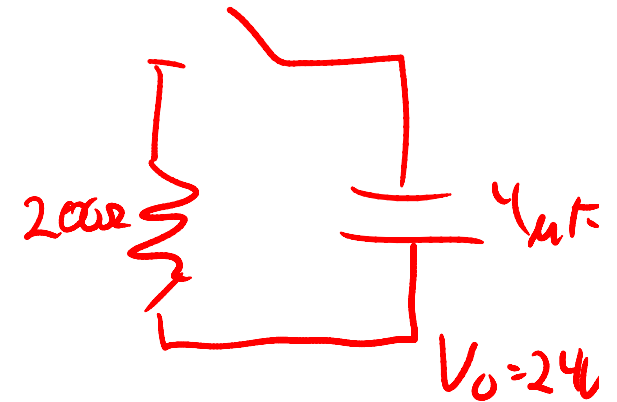c) What is time constant?

$$\begin{aligned}\tau_c &= RC = (200\Omega)(4\mu F) \\ &= 0.8\text{ms}\end{aligned}$$



Discharging example:


d) What is charge at $t=4\text{ms}$?



Discharging example:

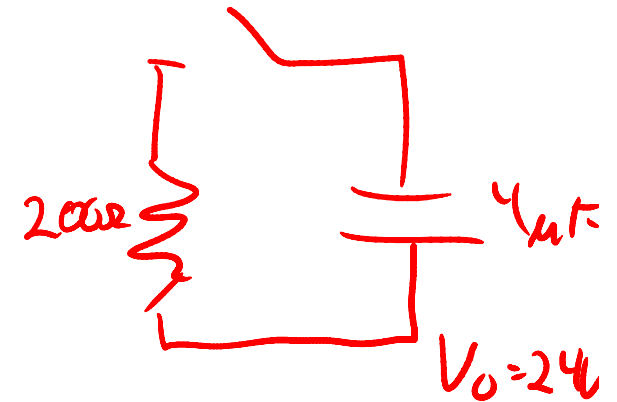d) What is charge at $t=4\text{ms}$?



$$\begin{aligned}q(4\text{ms}) &= Q_0 e^{-\frac{4\text{ms}}{0.8\text{ms}}} \\ &= 96\ \mu\text{C} e^{-5} \\ &= 0.647\ \mu\text{C}\end{aligned}$$




Voltage across an unknown capacitor in an RC circuit, every ten seconds after a switch in the circuit that allows the capacitor to discharge is closed. The capacitor was initially fully charged. Using the graph, estimate the time constant.

- ✓ 1. 7.5s
- 2. 15s
- 3. 30s
- 4. 45s
- 5. 60s

$$Q(\tau) = Q_0 e^{-\tau/\tau_c}$$

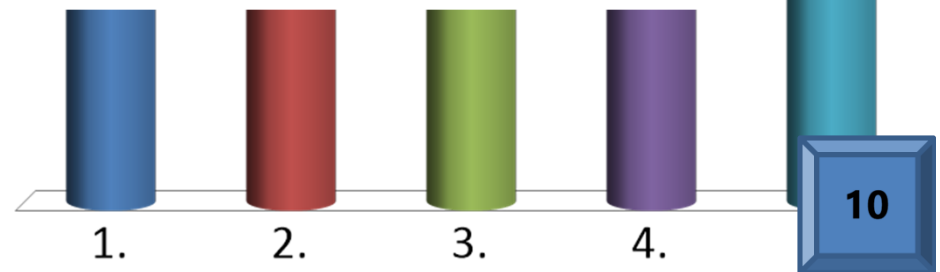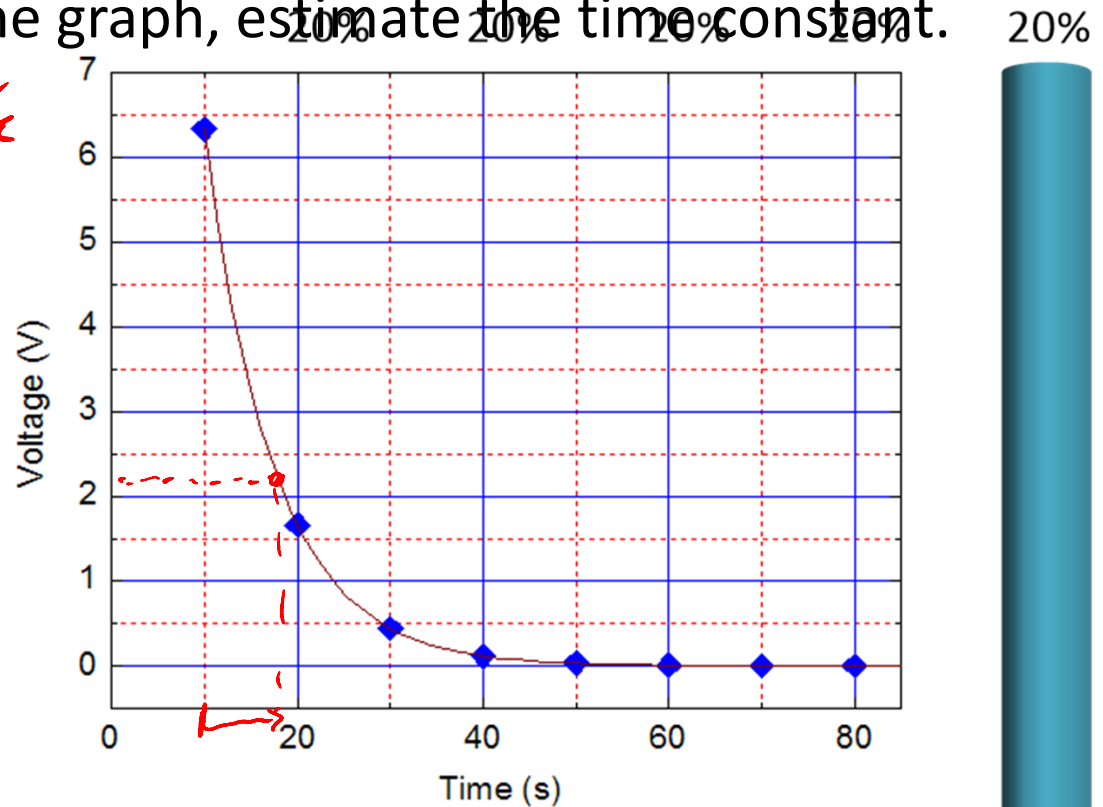

Response Counter

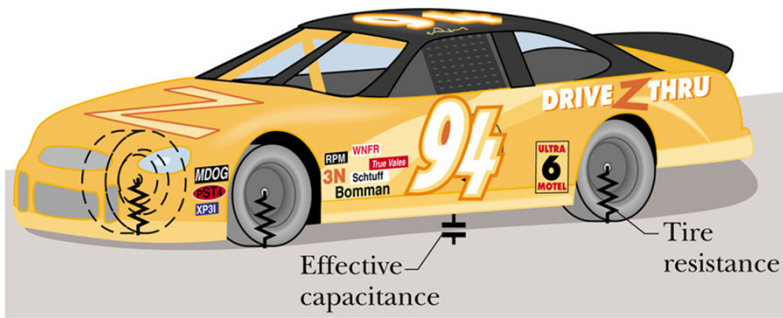


(a)


$$C_{\text{car/ground}} = 500 \text{ pF} \quad V_0 = 30 \text{ kV}$$

$$R_{\text{Tire}} = 100 \text{ G}\Omega \quad U_{\text{fire}} = 50 \text{ mJ}$$

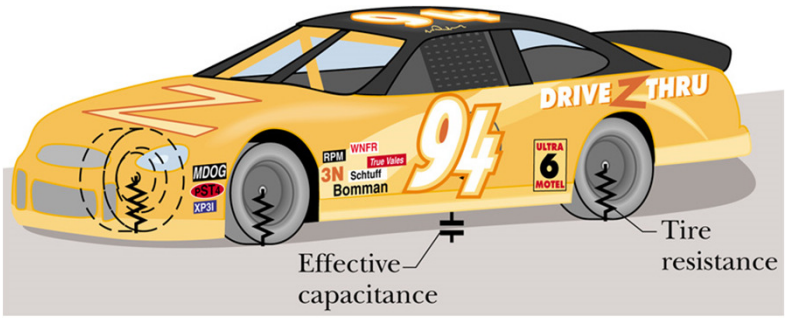
How long till you can safely
refuel, till the energy stored in the
static electricity won't ignite the gas?



(a)

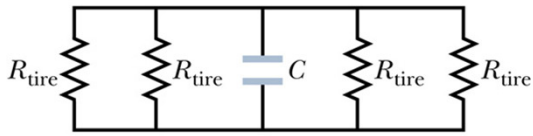


(b)

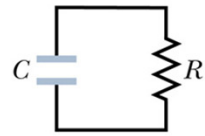


(c)

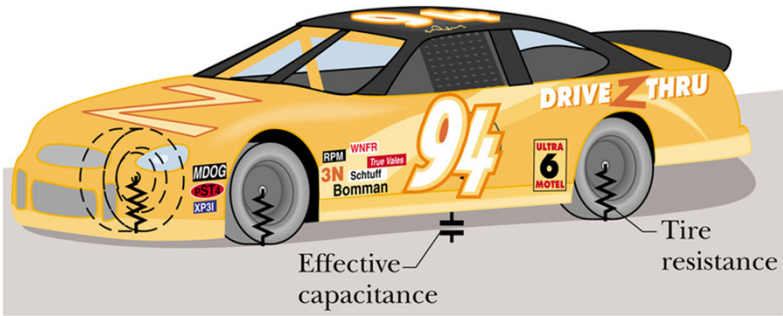First, draw it as a circuit & simplify it




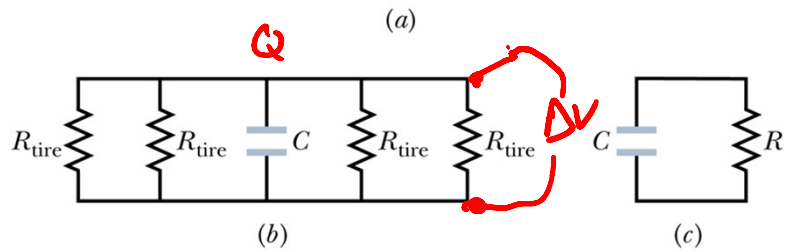First, draw it as a circuit & simplify it




4 tires in parallel
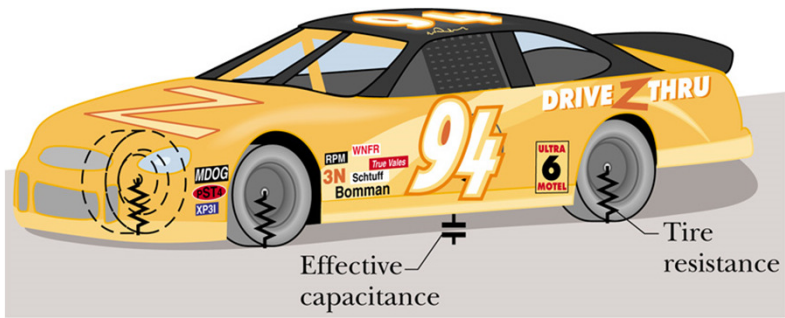
$$\frac{1}{R_{eq}} = 4 \left(\frac{1}{R_{Tire}} \right) \quad R_{eq} = 25 \text{ G}\Omega$$




(a)

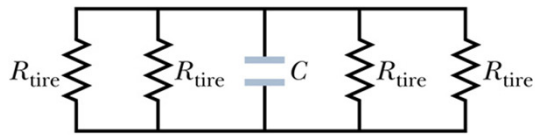
What's U_{cap} , and how does that look as a function of time?




(b)

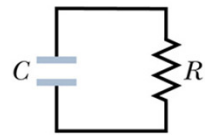


(c)

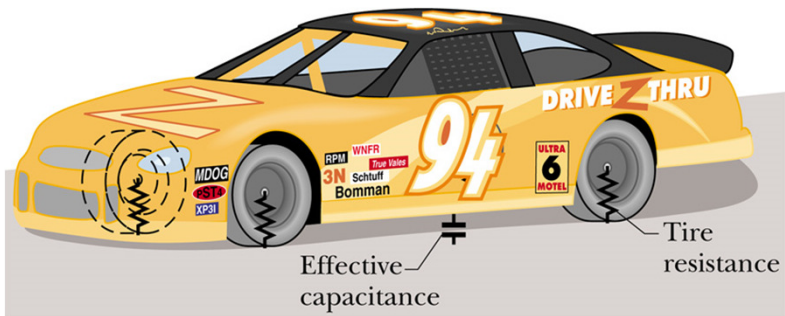

(a)

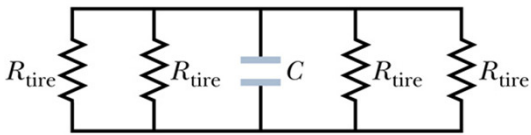

(b)

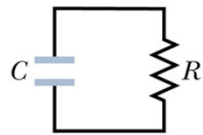

(c)

What's U_{cap} , and how does that look as a function of time?


$$U = \frac{Q^2}{2C}$$

$$U(t) = \frac{Q^2(t)}{2C}$$

$$= \frac{Q_0^2}{2C} e^{-2t/RC}$$


$$U(t) = \frac{(CV_0)^2}{2C} e^{-2t/RC}$$

$$= \frac{CV_0^2}{2} e^{-2t/RC}$$

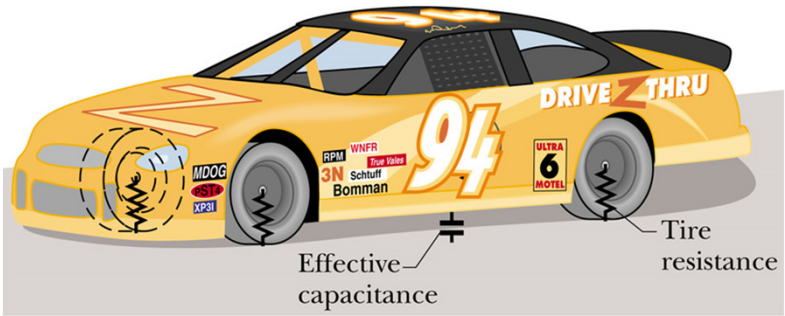


(a)

Solve for t

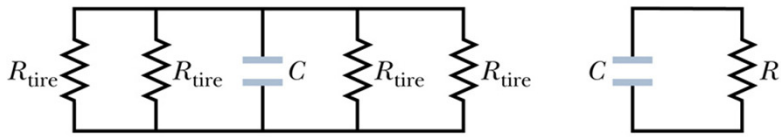


(b)


(c)

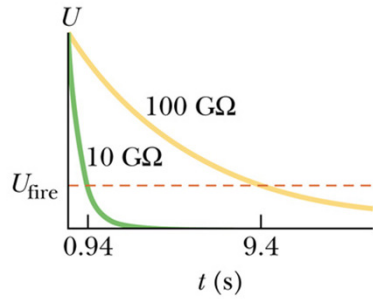

(d)

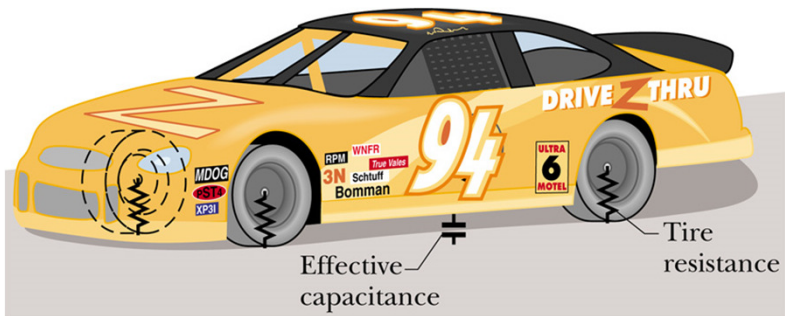


(a)

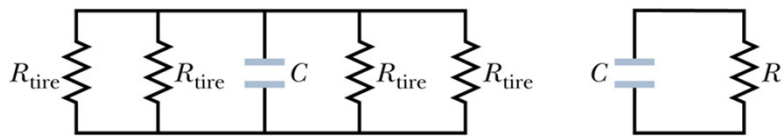

(b)

(c)

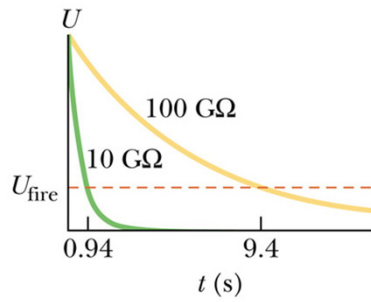

(d)


Solve for t

$$U_{\text{exp}} = \frac{CU_0^2}{2} e^{-2t/RC}$$

$$\ln\left(\frac{2U_{\text{exp}}}{CU_0^2}\right) = -\frac{2t}{RC}$$


$$t = -\frac{RC}{2} \ln\left(\frac{2U_{\text{exp}}}{CU_0^2}\right)$$

$$t = 9.4 \text{ s}$$

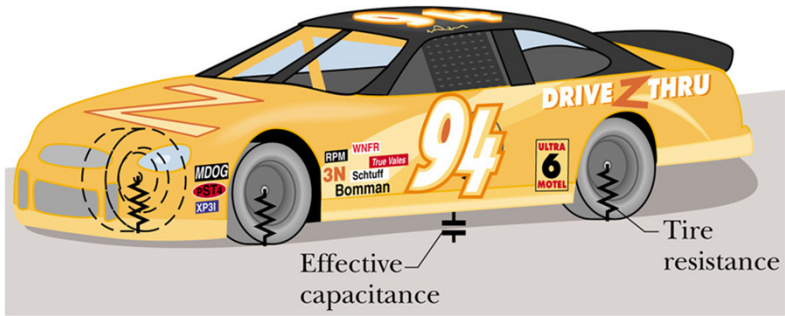


(a)

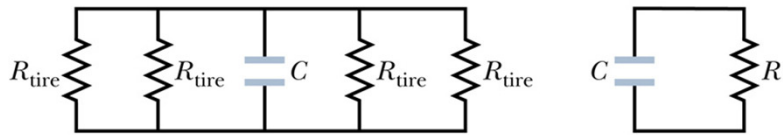How to reduce that time, to allow for faster pit stops?




(b)


(c)

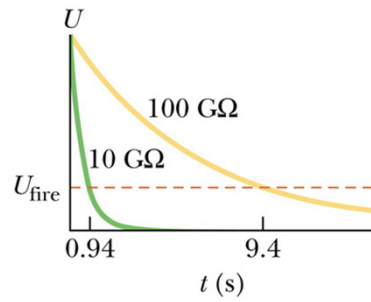


(d)

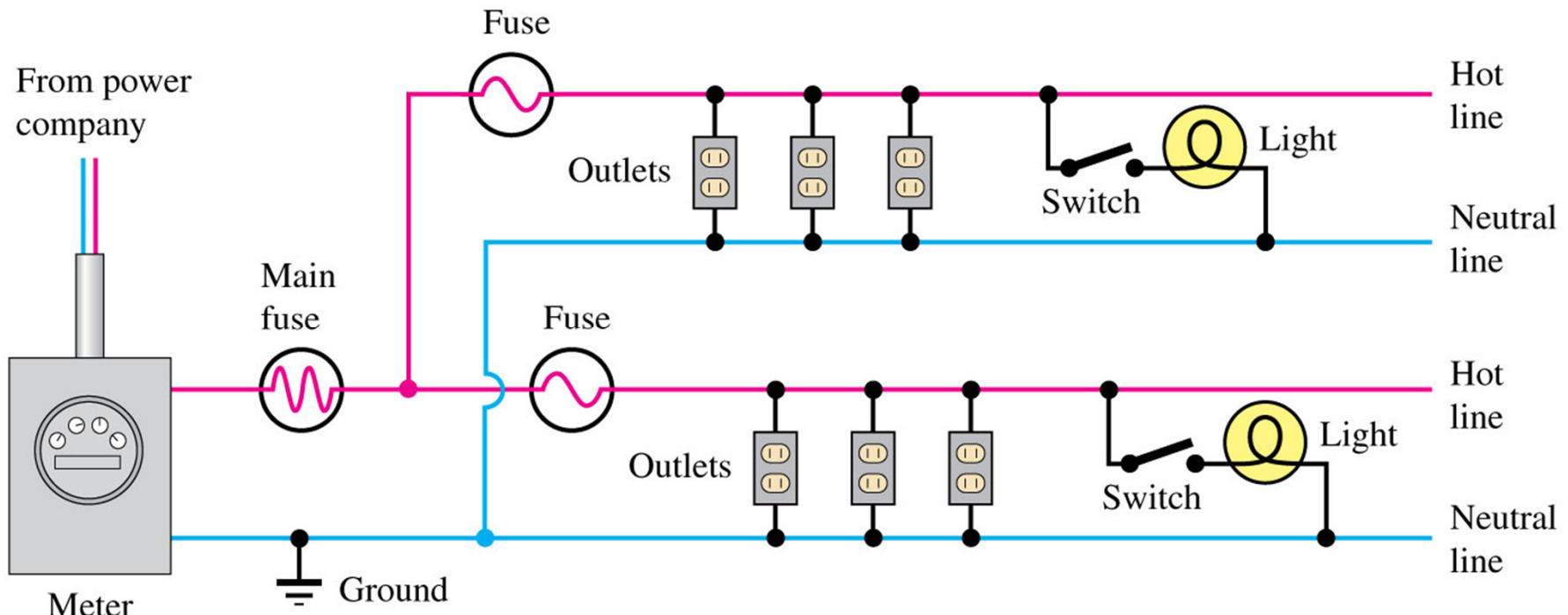


(a)

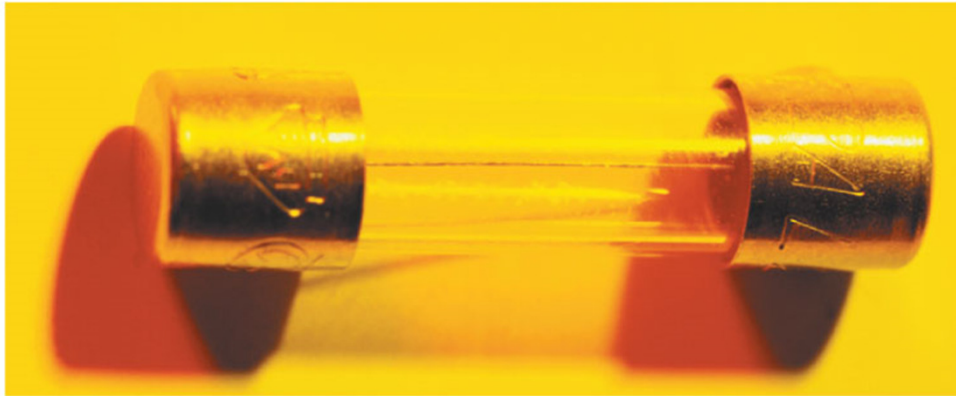

(b)

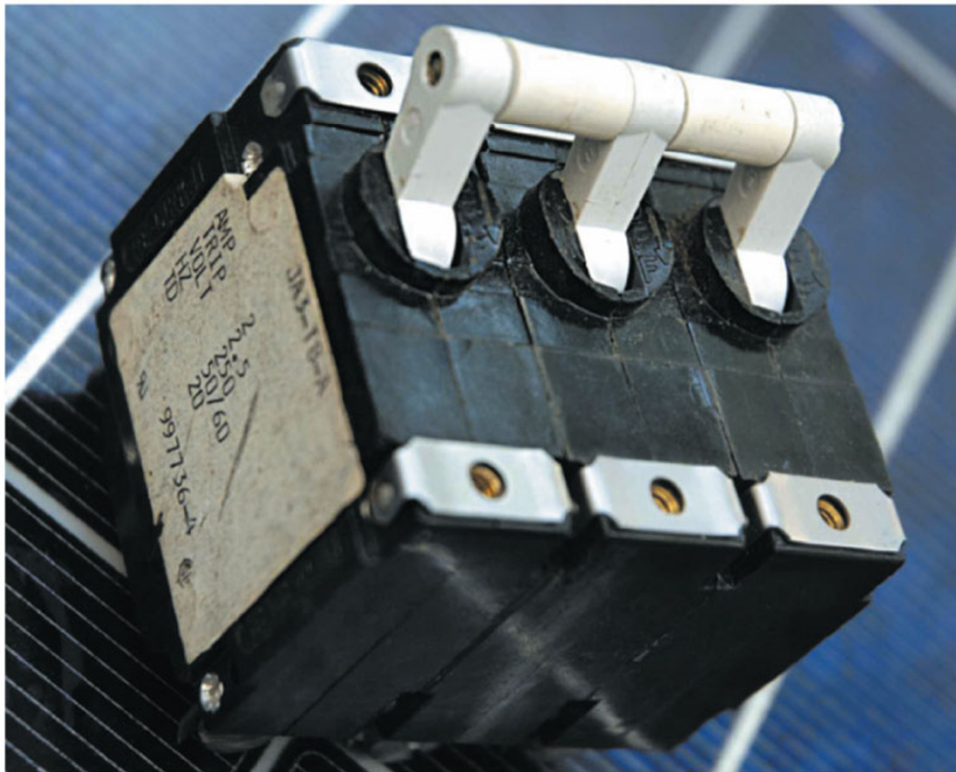

(a) Two-prong plug

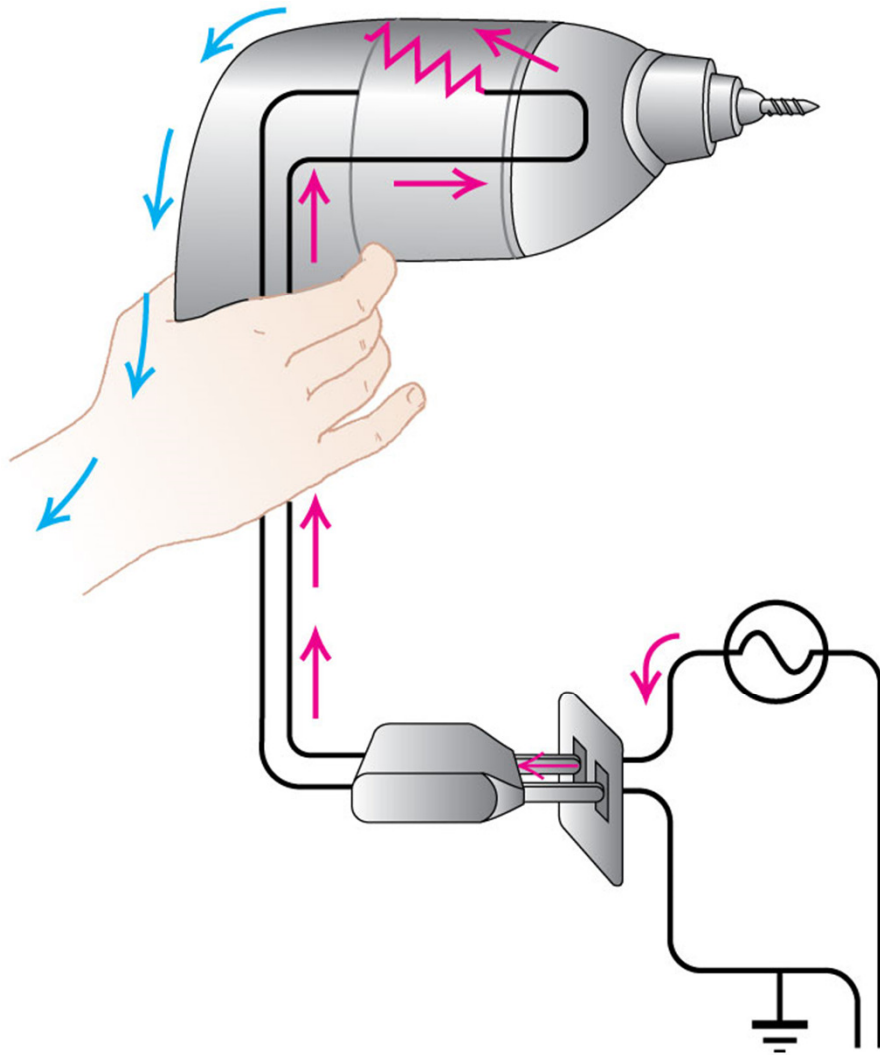

(b) Three-prong plug

