

Week #5 Homework

1. Verify that an 8°C rise in ambient temperature will cause a base-voltage biased common-emitter amplifier to saturate, assuming that it was initially biased for $V_C=0.5 V_{CC}$. Draw this out using only the r_E inherent in the transistor (don't add an extra R_E or R'). "Saturate" means that so much current flows that V_{CE} gets to only about 0.1V .
2. Design a tuned common-emitter amplifier to operate at 100 kHz : a bandpass filter built into the stuff stuck onto the transistor's emitter such that one frequency gets amplified by the amp, others do not. Use a bypassed emitter resistor, and set the quiescent current at 1.0 mA . Assume $V_{CC}=+15\text{ V}$ and $L=1.0\text{ mH}$, and put a 6.2k resistor across the LC to set $Q=10$ (to get a 10% bandpass: look in your notes from when we first put up a passive LRC filter). Use capacitive input coupling.
3. Design a common-emitter npn amplifier with a voltage gain of 15, V_{CC} of $+15\text{ V}$, and an I_C of 0.5 mA . Bias the collector at $0.5 V_{CC}$, and put the low-frequency 3dB point at 100 Hz .